

Electrical Science - I

(IEC-102)


Lecture-02

Types of Circuit Elements


Types of Circuit Elements

Circuit Elements


Types of Circuit Elements

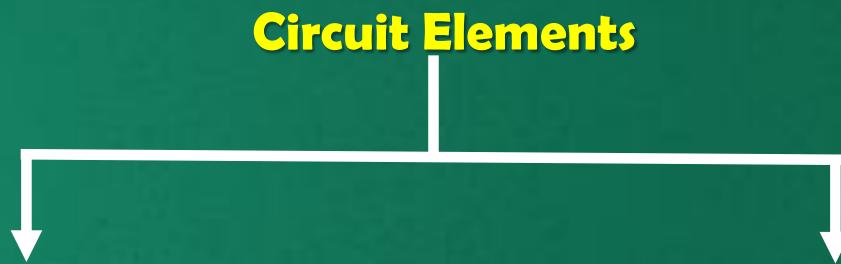


Types of Circuit Elements

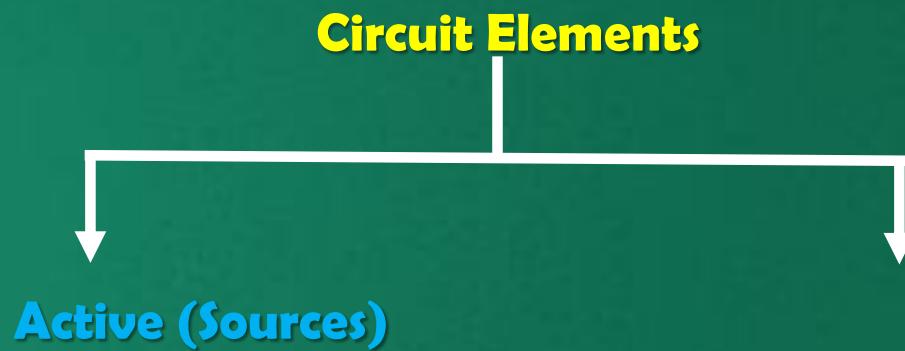


Types of Circuit Elements

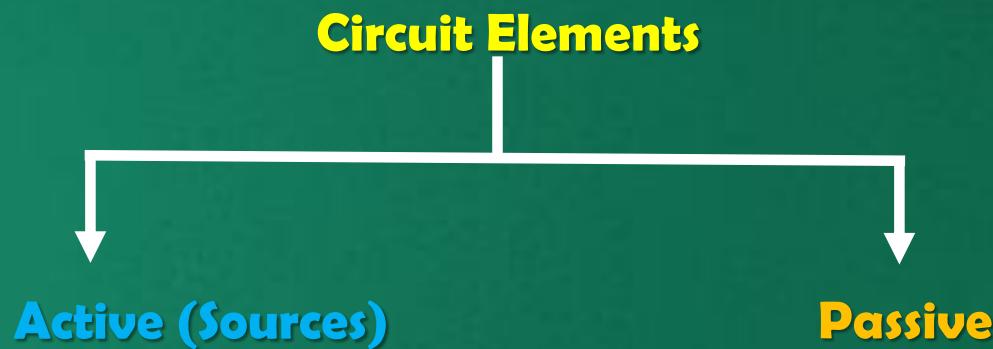


Types of Circuit Elements

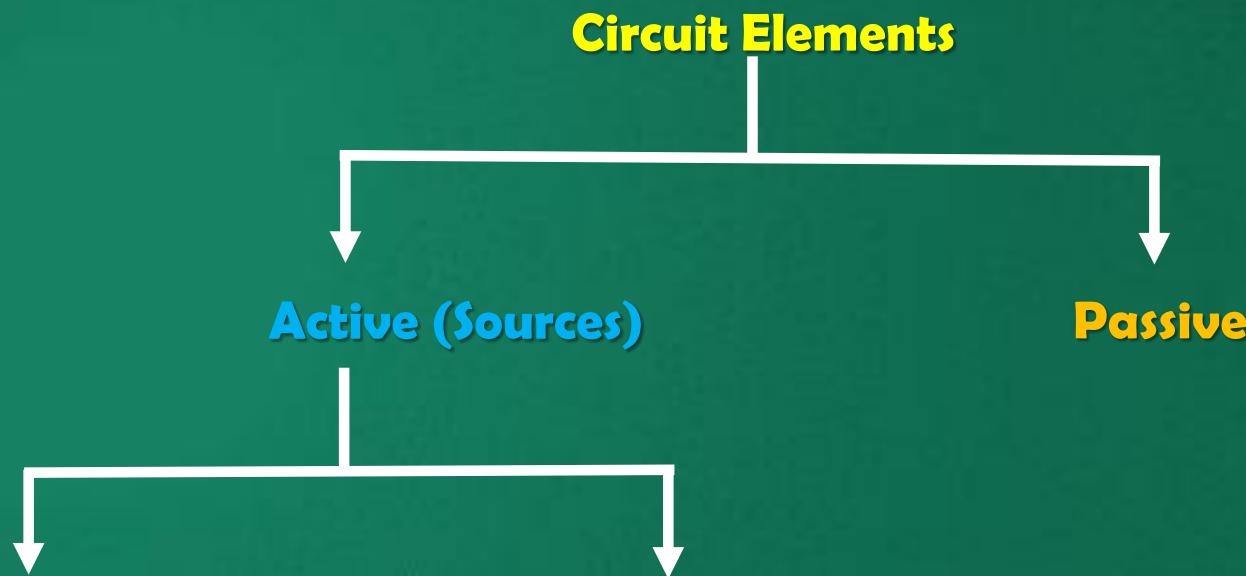


Types of Circuit Elements

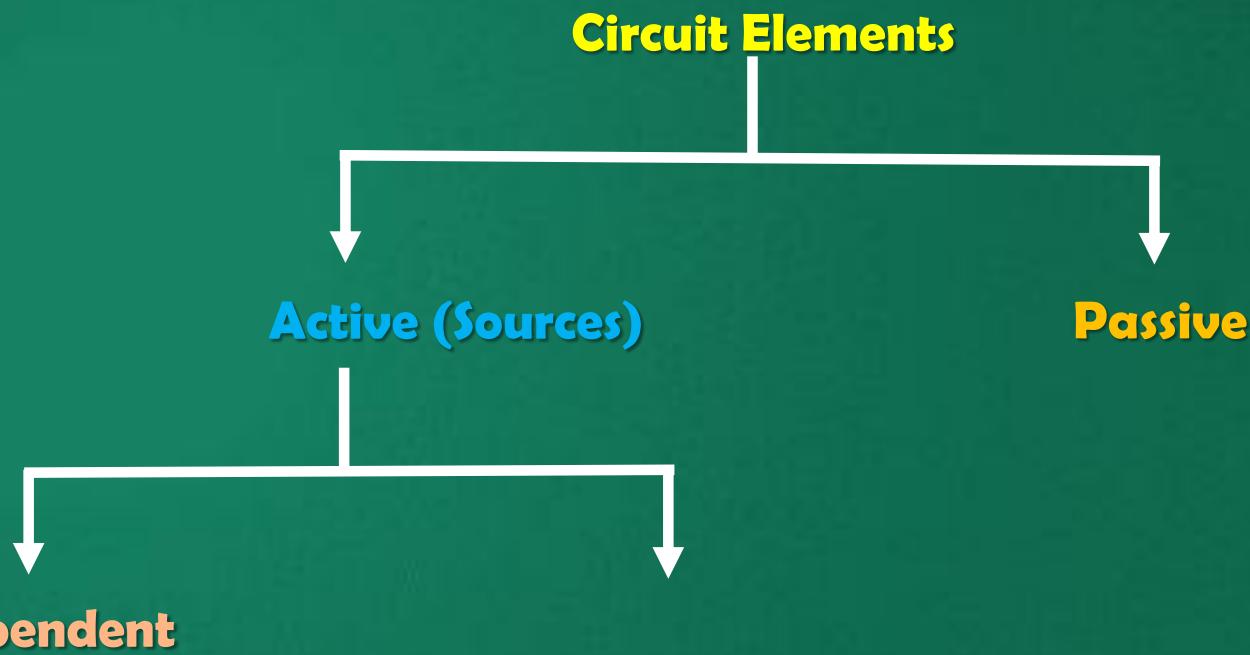


Types of Circuit Elements

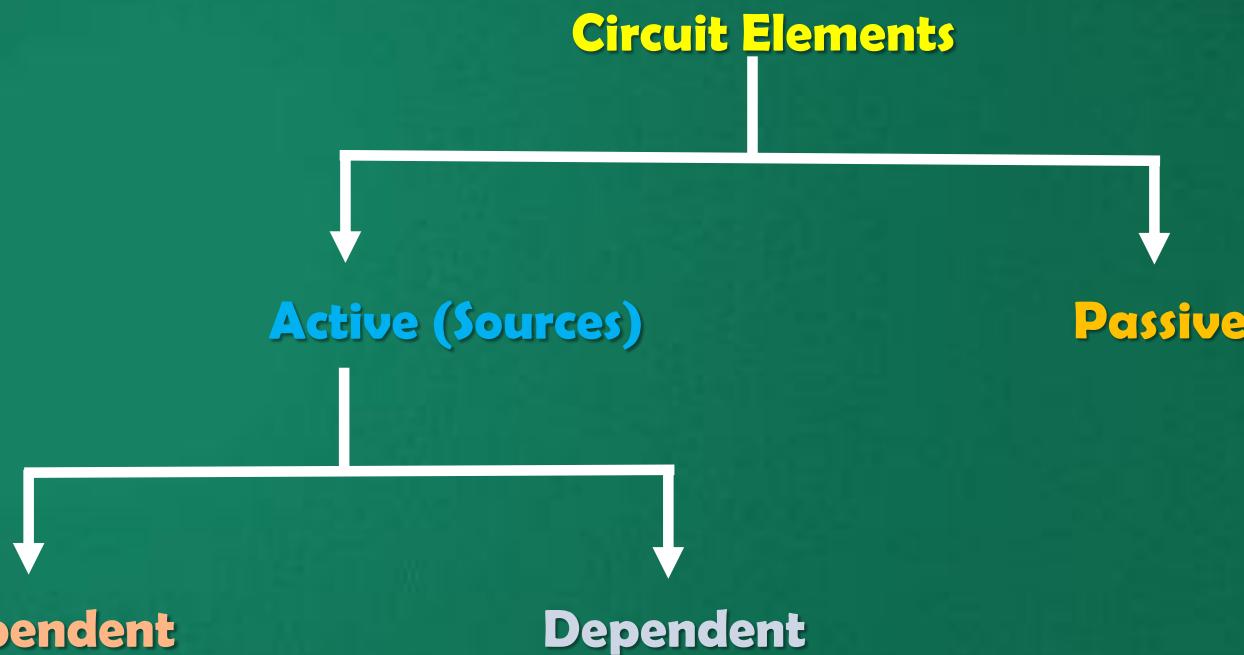


Types of Circuit Elements

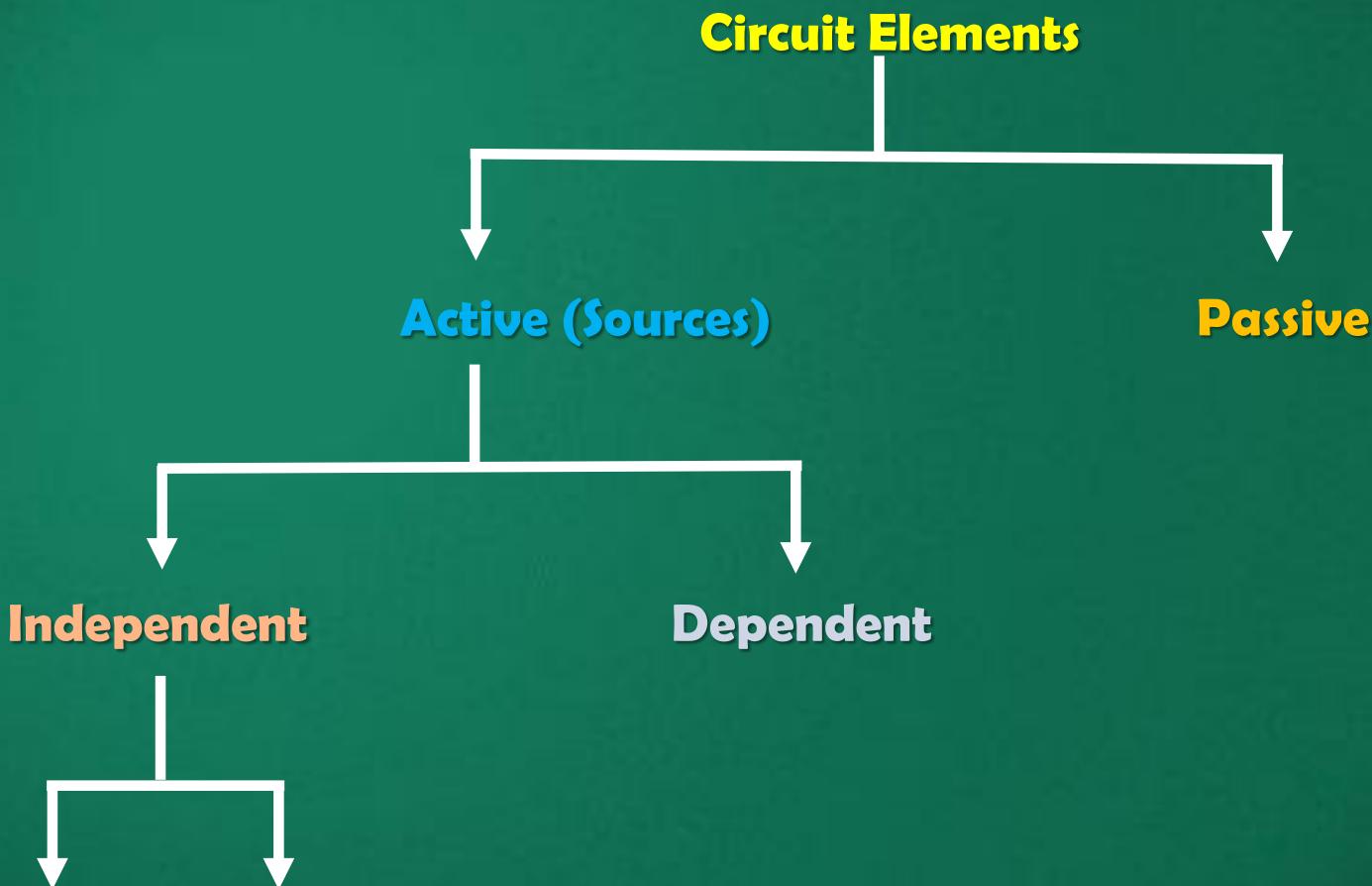


Types of Circuit Elements

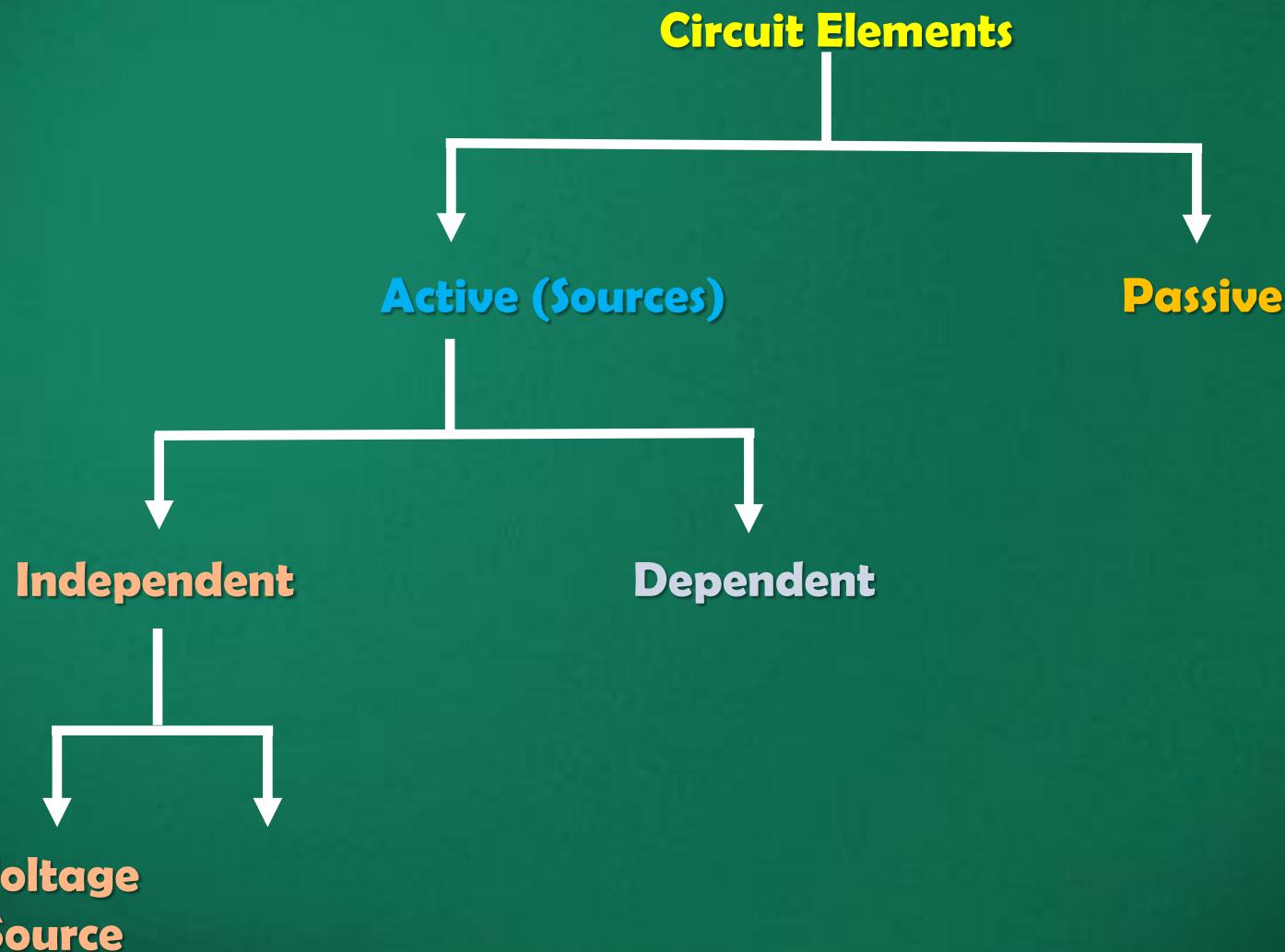


Types of Circuit Elements

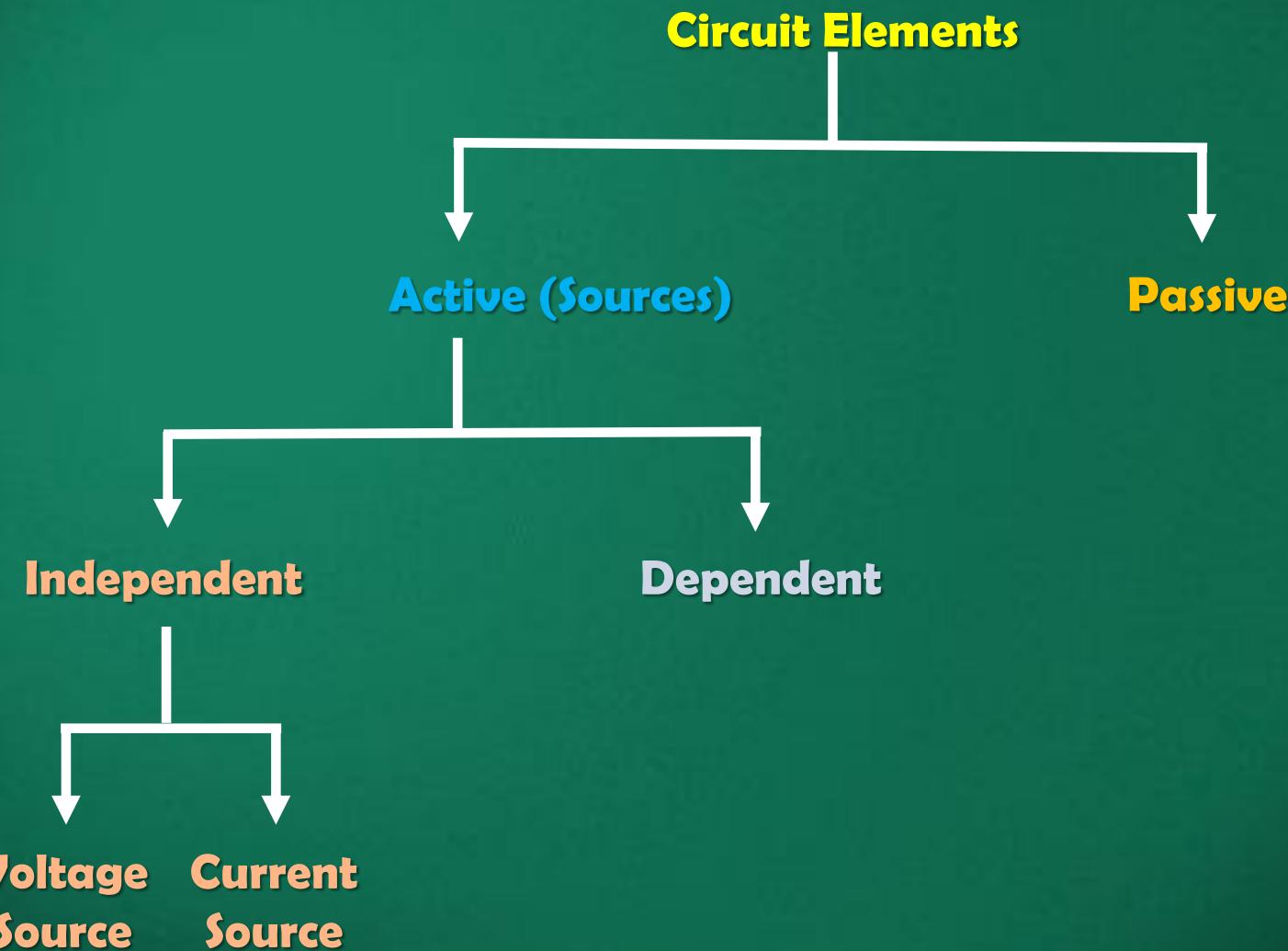


Types of Circuit Elements

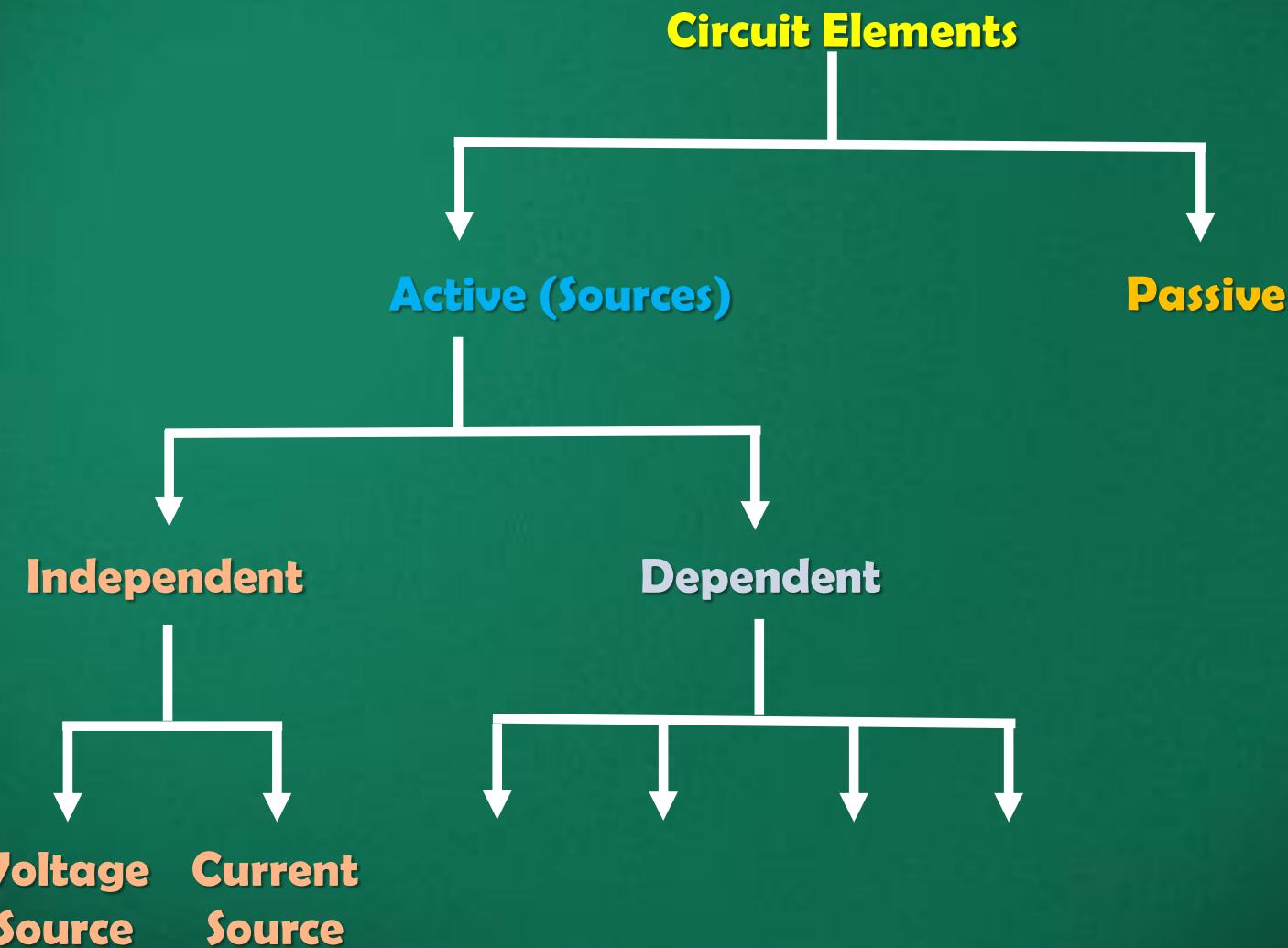


Types of Circuit Elements

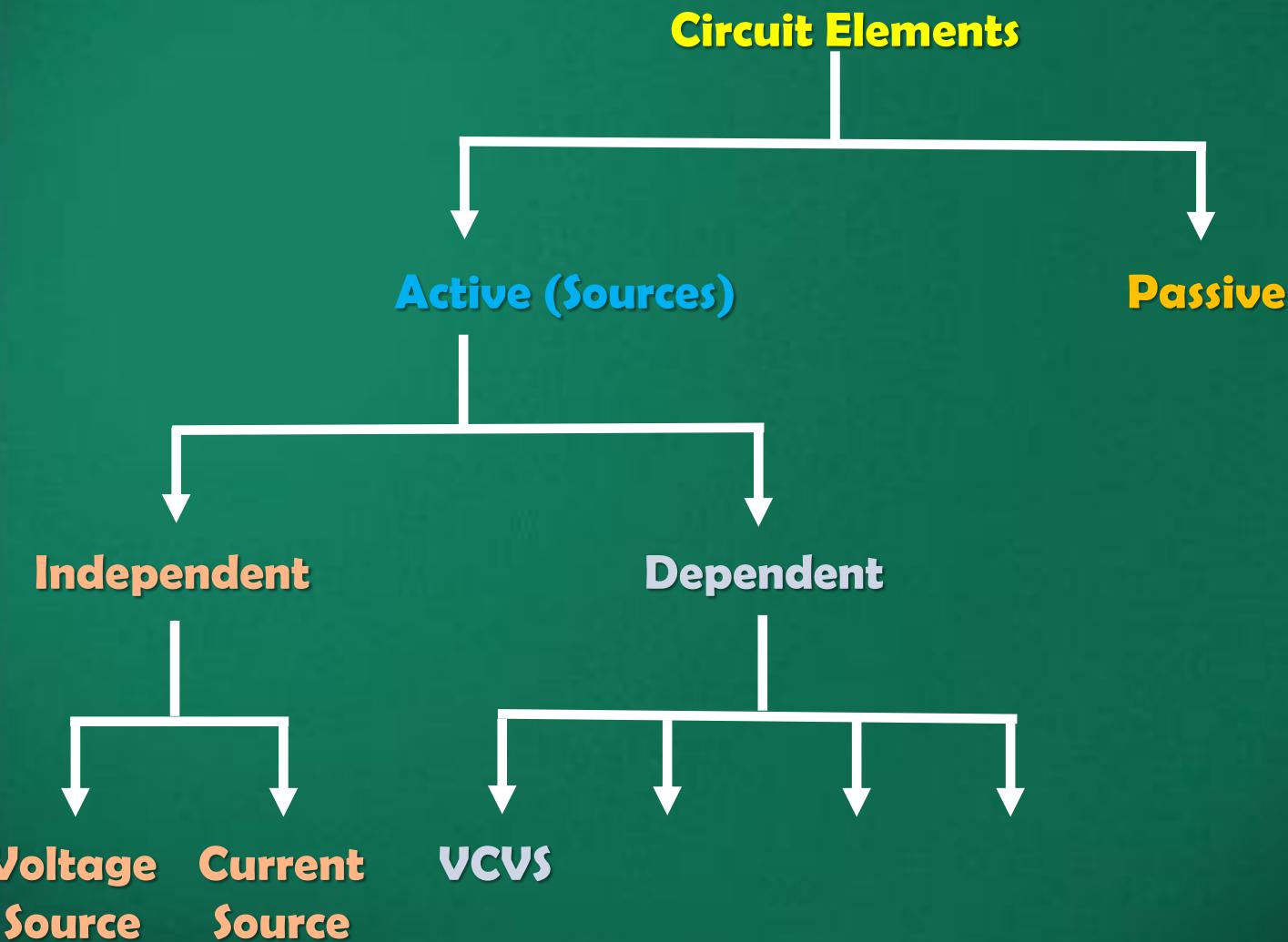

Types of Circuit Elements

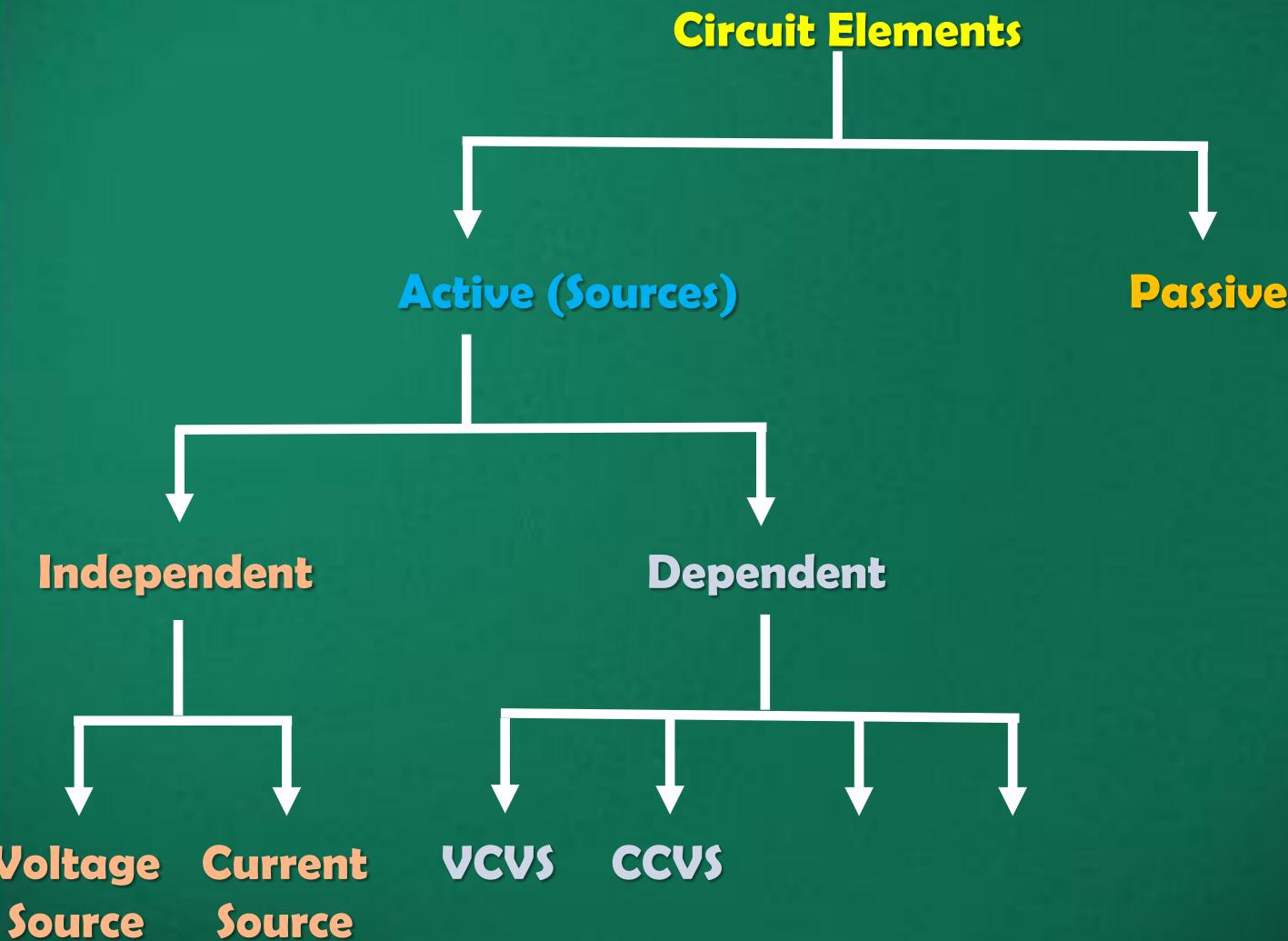


Types of Circuit Elements

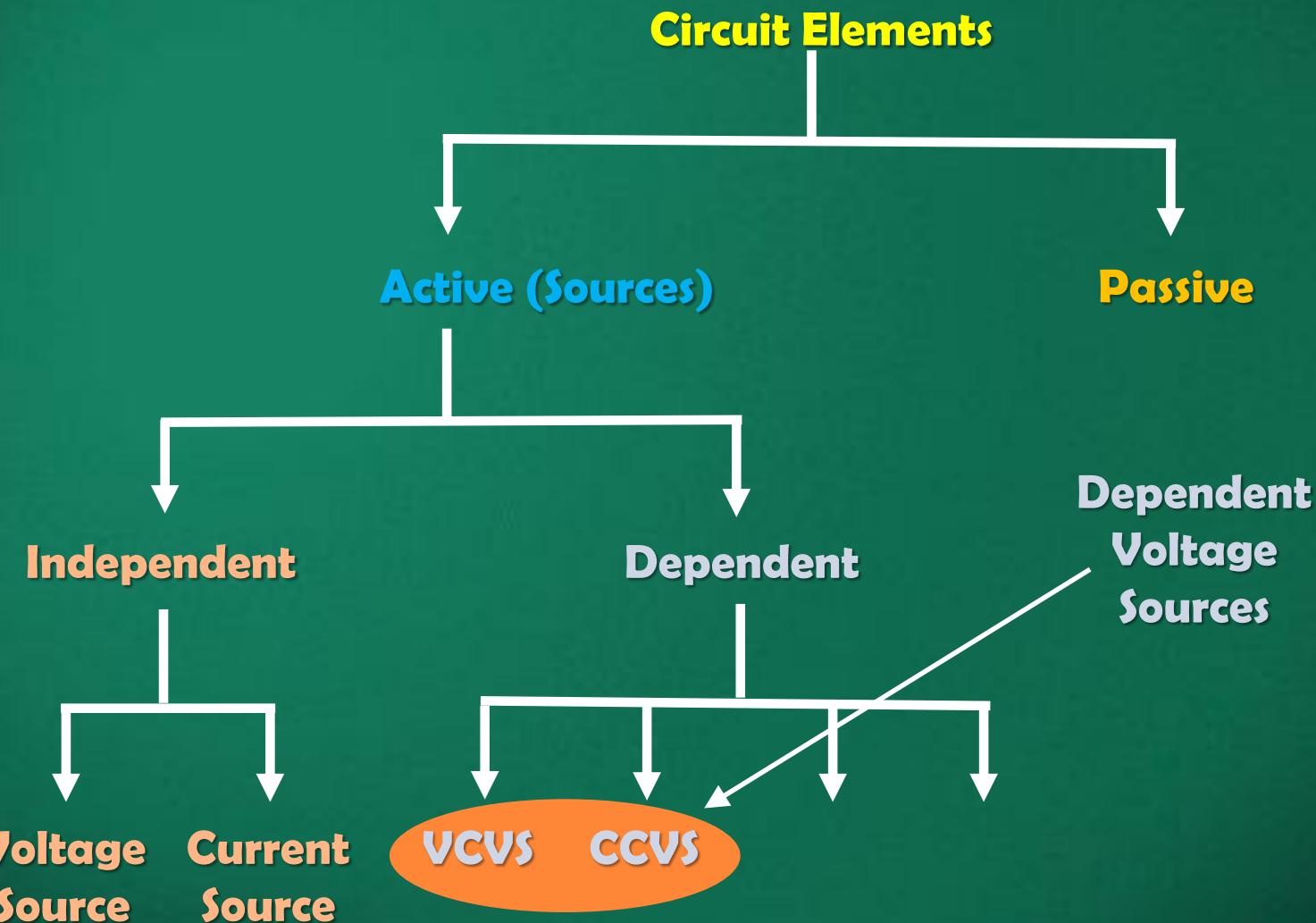


Voltage Source Current Source


Types of Circuit Elements

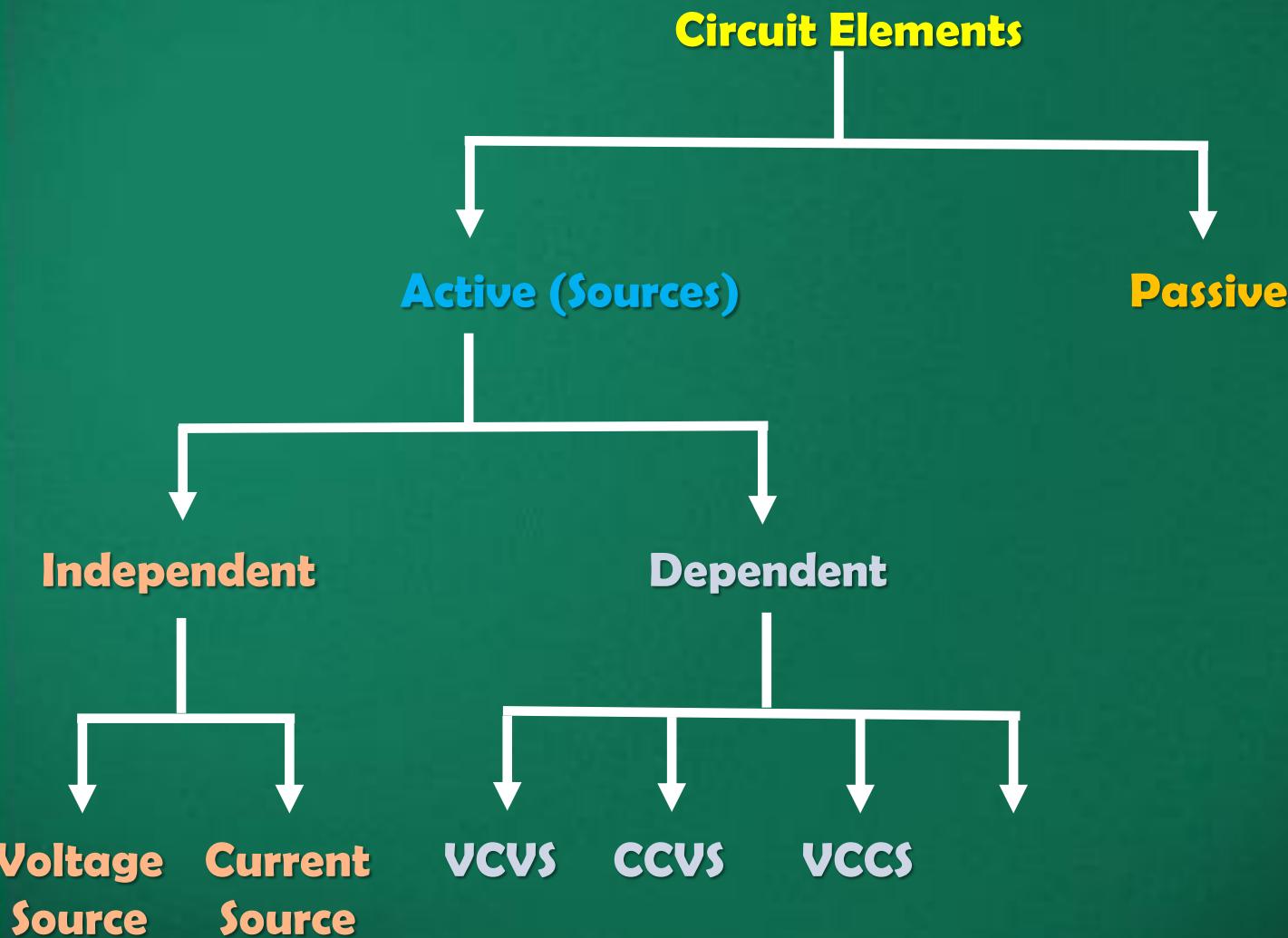


Types of Circuit Elements

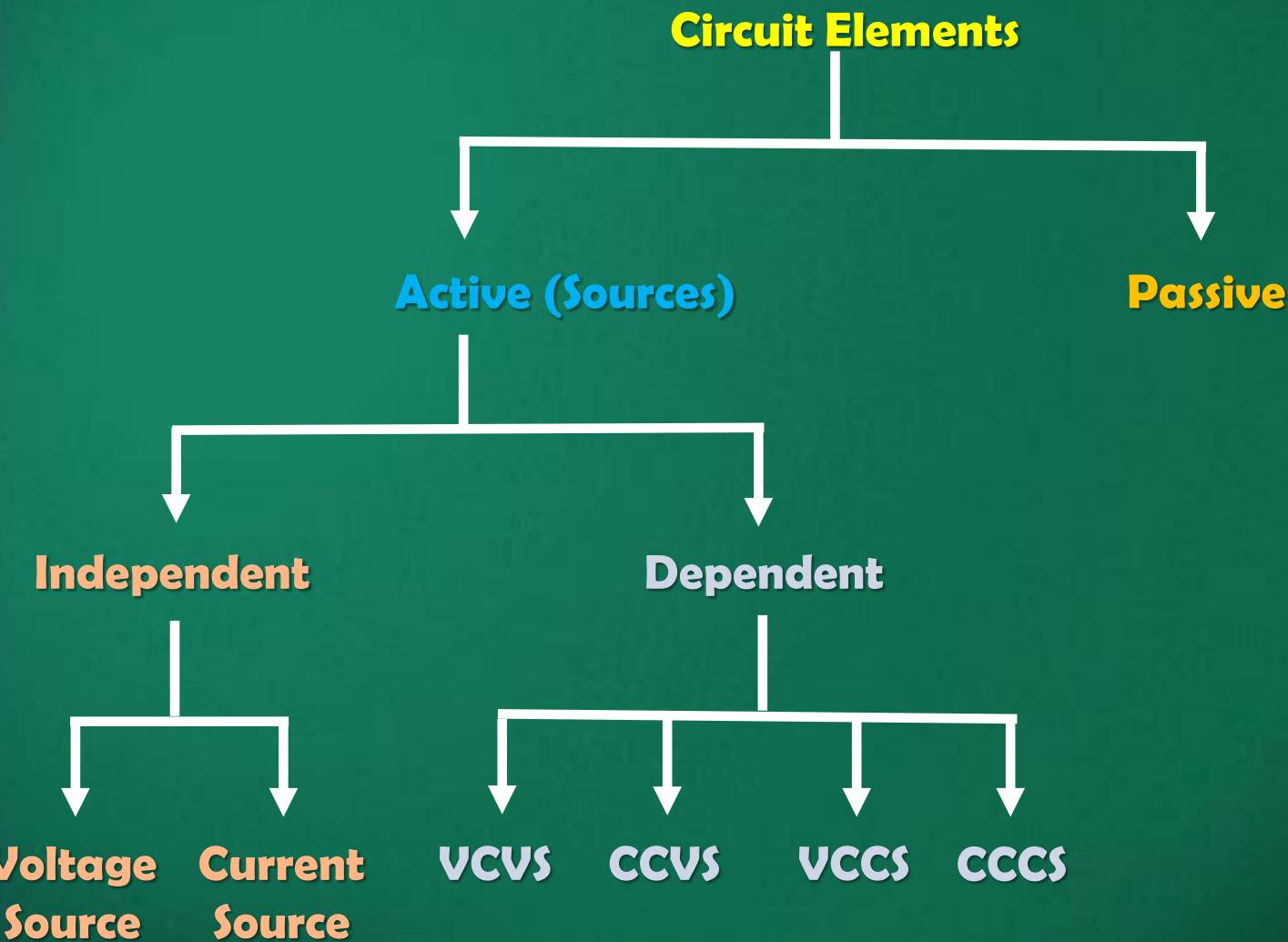


Types of Circuit Elements

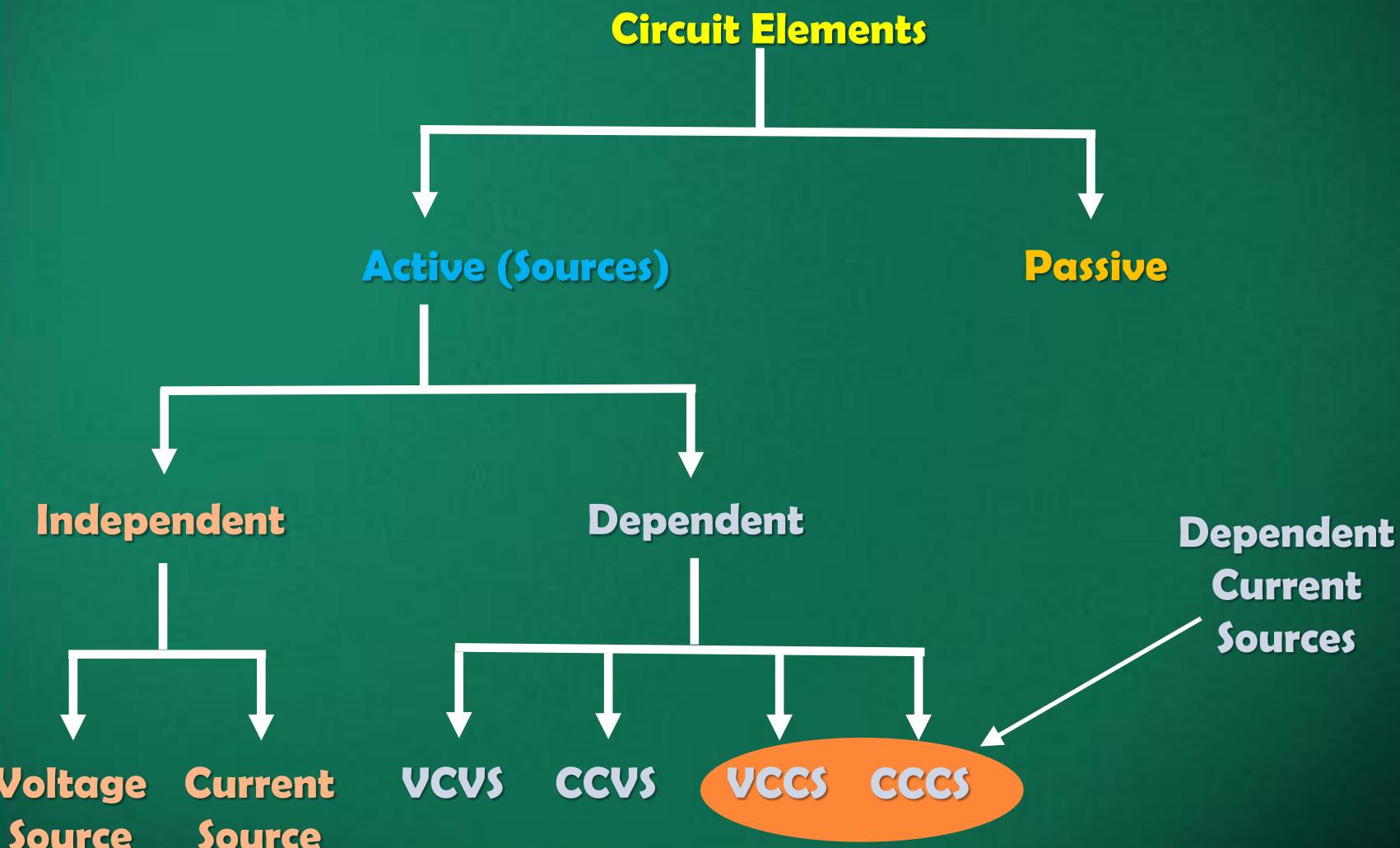


Types of Circuit Elements

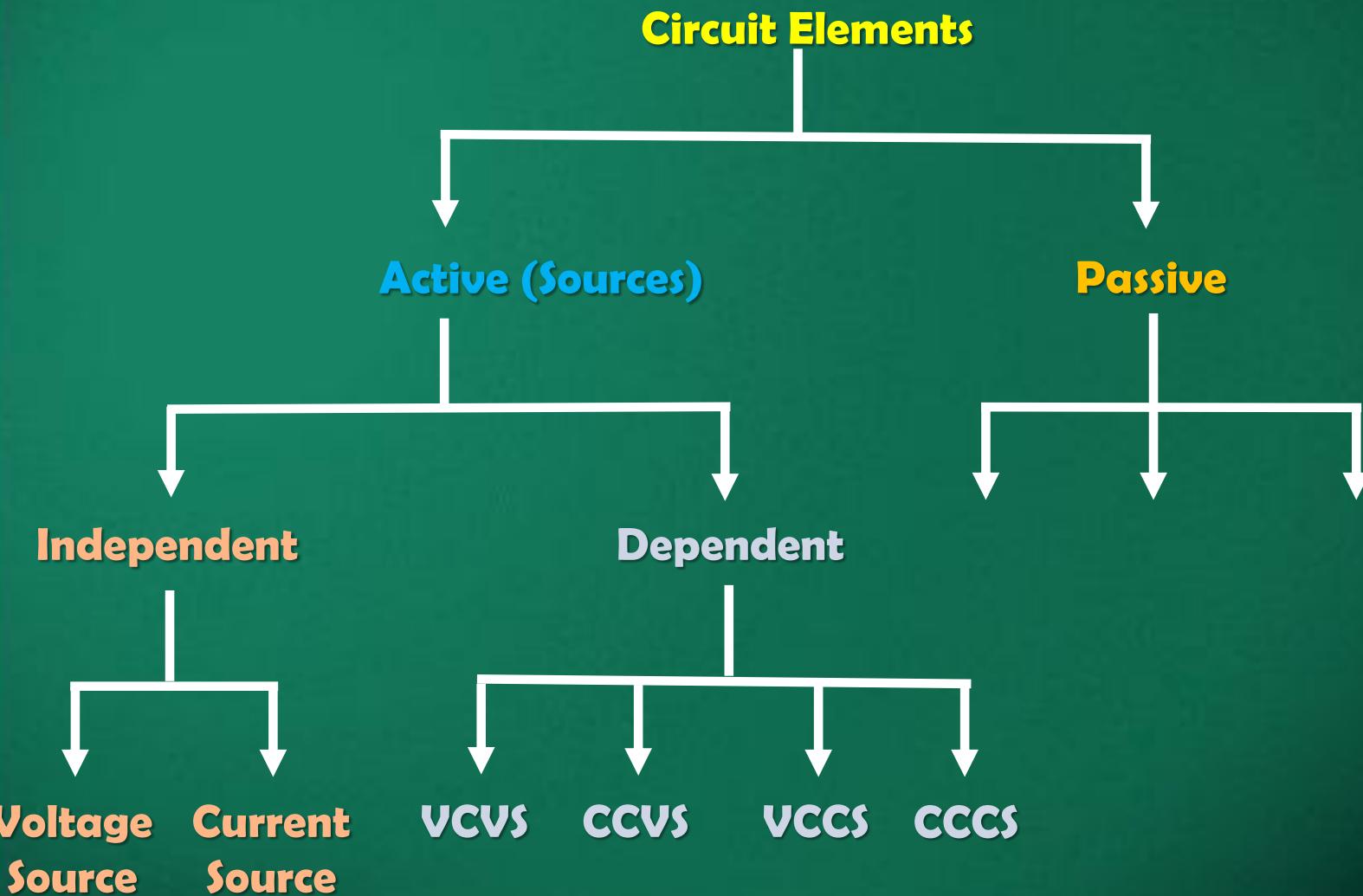


Types of Circuit Elements

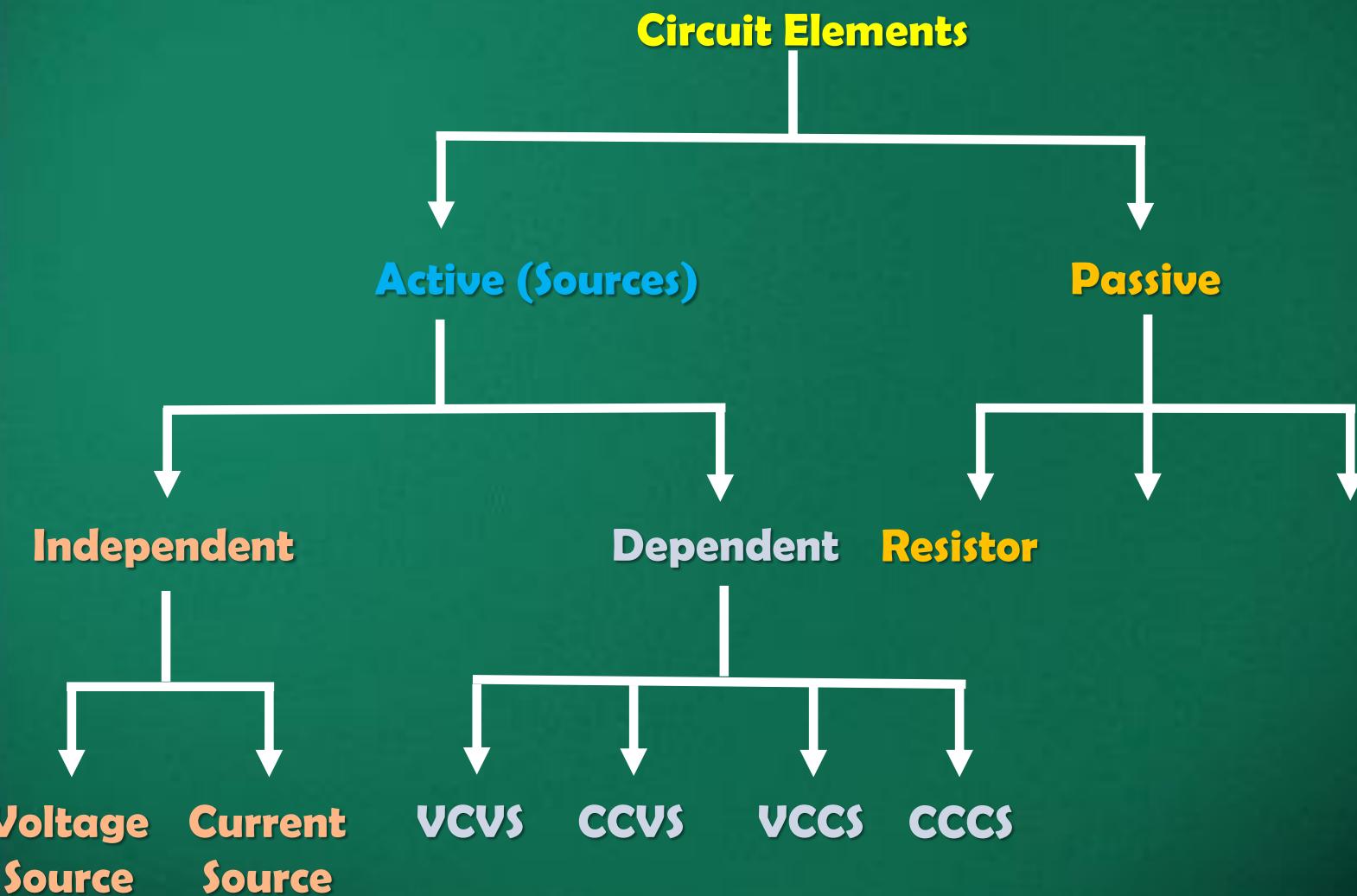

Types of Circuit Elements

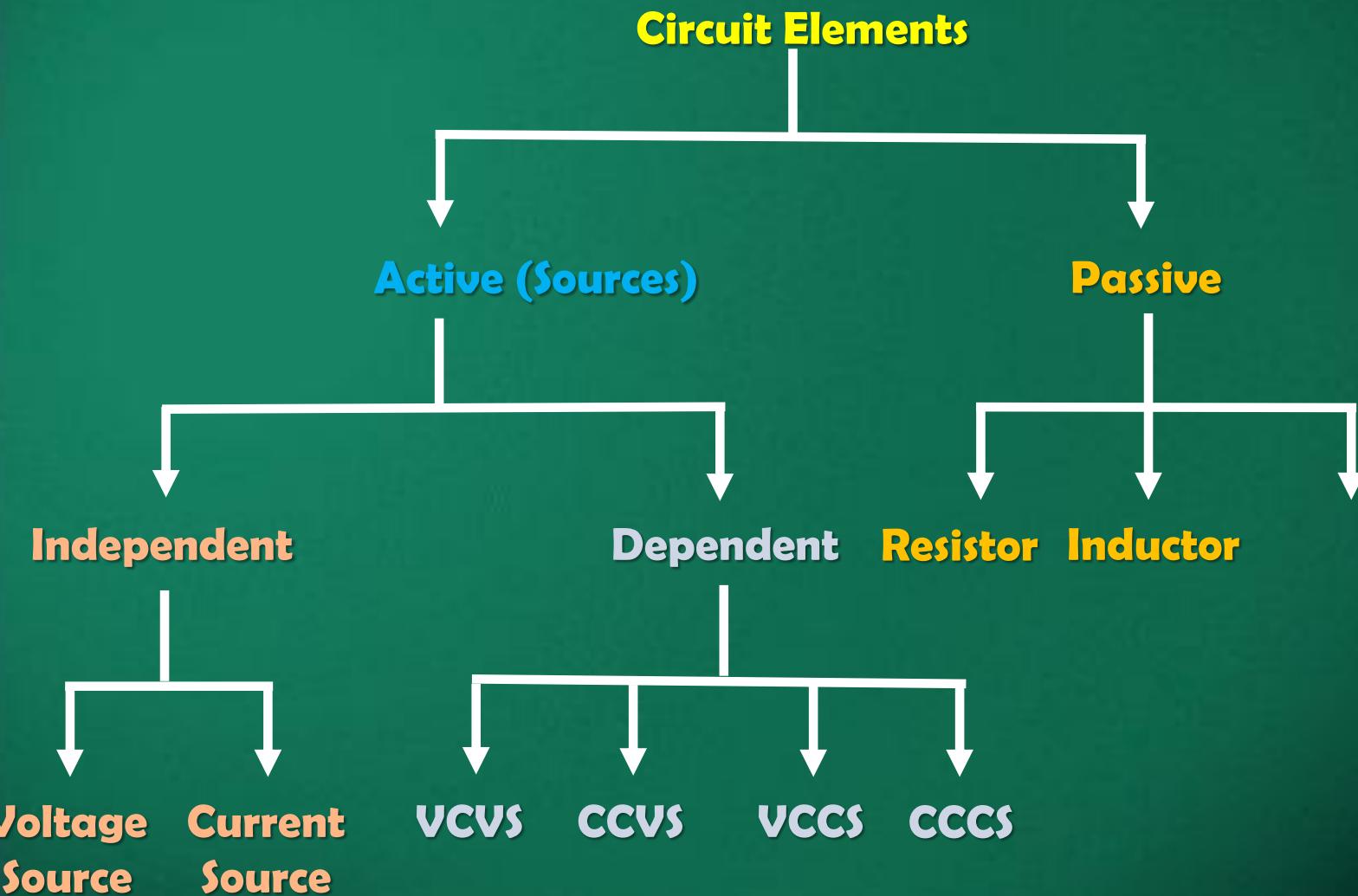

Types of Circuit Elements

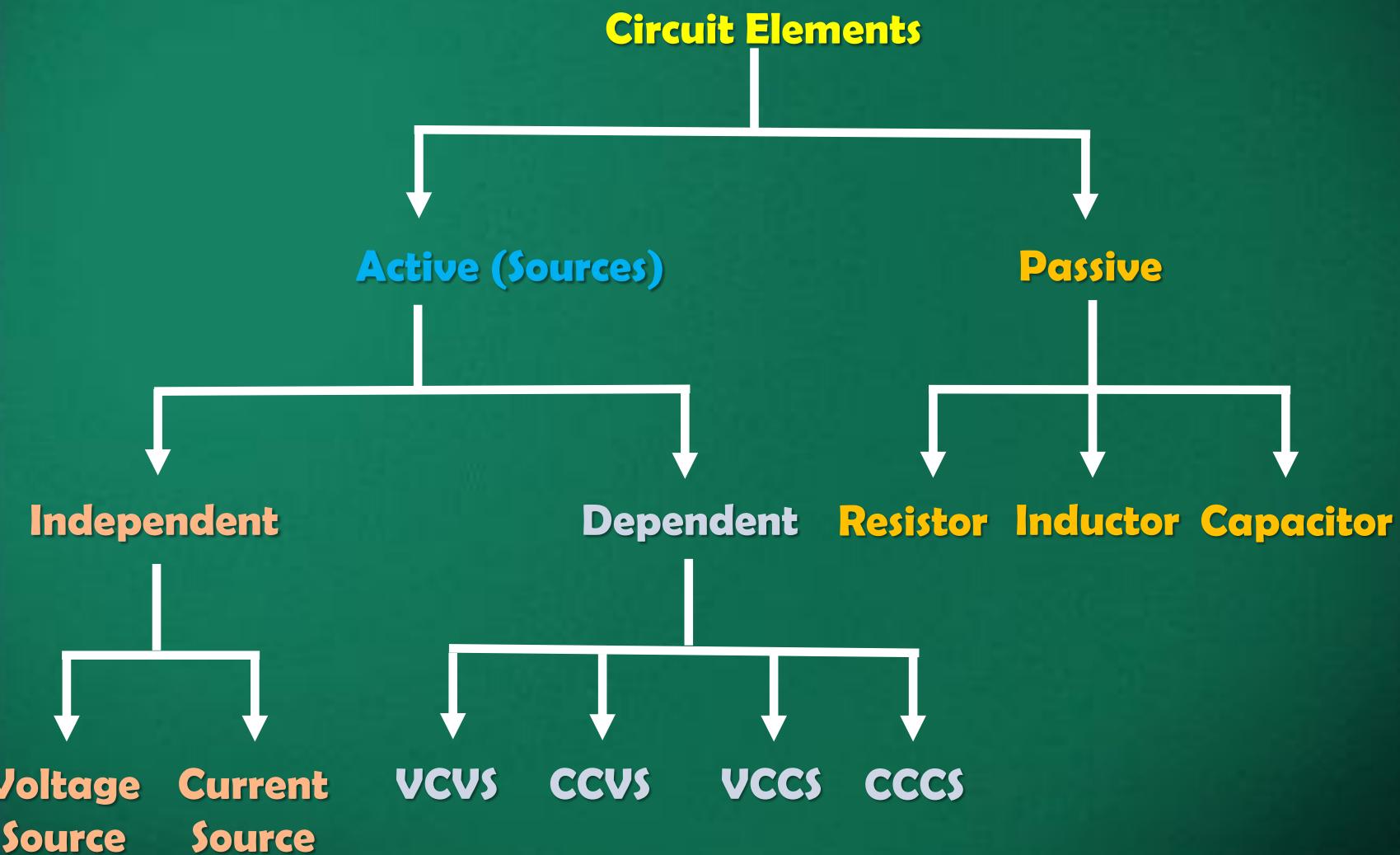

Networks and Circuits

Network is an interconnection of two or more simple elements.

Networks and Circuits

Network is an interconnection of two or more simple elements.

If a network contains at least one closed path, it is called an electric circuit.

Networks and Circuits

Network is an interconnection of two or more simple elements.

If a network contains at least one closed path, it is called an electric circuit.

Note: Every circuit is a network, but not all networks are circuits.

Networks and Circuits


Network is an interconnection of two or more simple elements.

If a network contains at least one closed path, it is called an electric circuit.


Note: Every circuit is a network, but not all networks are circuits.

The elements in a network/circuit are connected to each other by wire.

Networks and Circuits


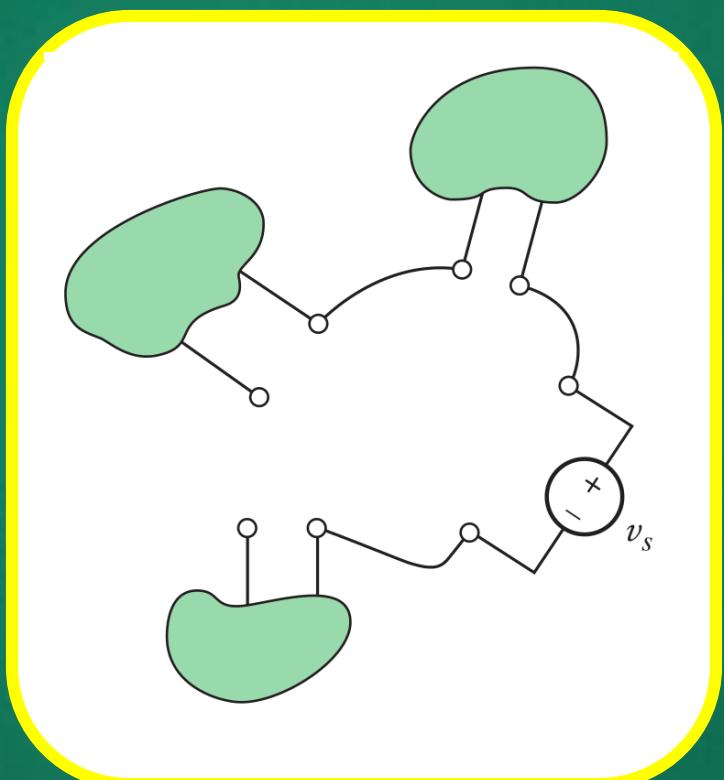


Networks and Circuits

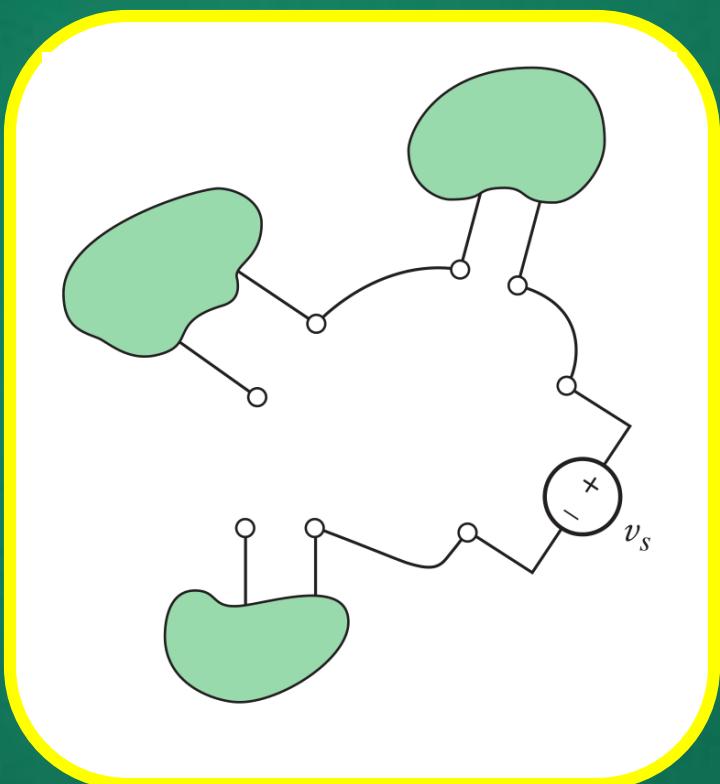


A network that is
not a circuit.

Networks and Circuits

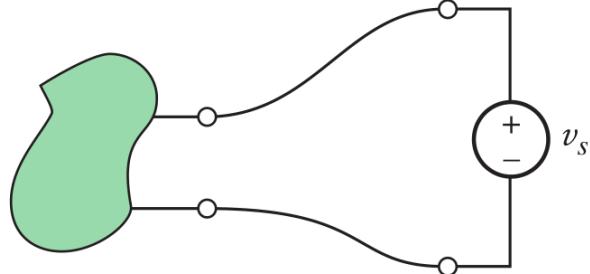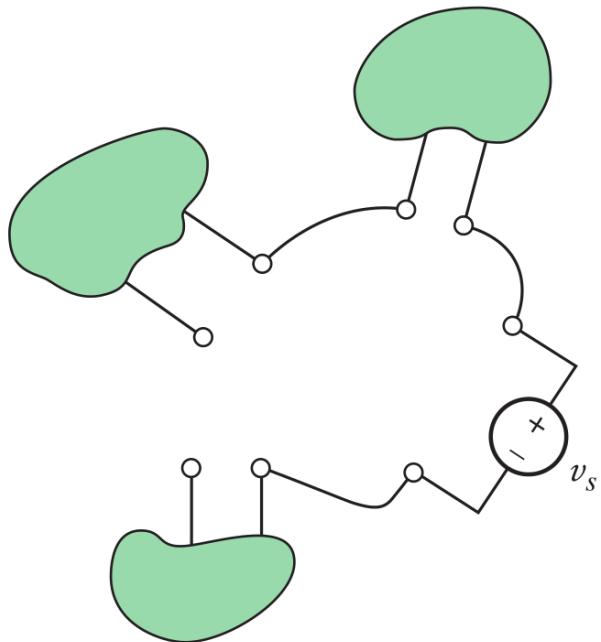


A network that is
not a circuit.

Networks and Circuits

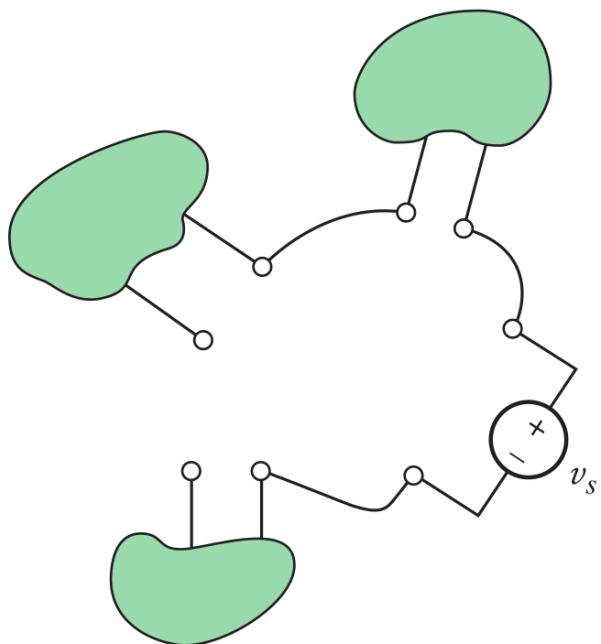

A network that is
not a circuit.

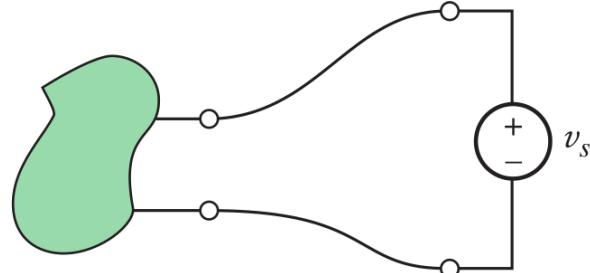

A network that is
a circuit.

Linear Circuit

A circuit which consists only linear passive elements and linear dependent sources is termed as a linear circuit.

Circuit Terminology

Circuit Terminology

Node – A point at which two or more elements have a common connection.

Circuit Terminology

Node – A point at which two or more elements have a common connection.

Path – When we pass through nodes without encountering a node more than once is called a path.

Circuit Terminology

Node – A point at which two or more elements have a common connection.

Path – When we pass through nodes without encountering a node more than once is called a path.

Loop – Loop is a closed path. We end up at the same node at which we start.

Circuit Terminology

Node – A point at which two or more elements have a common connection.


Path – When we pass through nodes without encountering a node more than once is called a path.

Loop – Loop is a closed path. We end up at the same node at which we start.

Branch – It is a single path in a network, composed of one simple element and a node at each end of the element. A branch represents a single element.

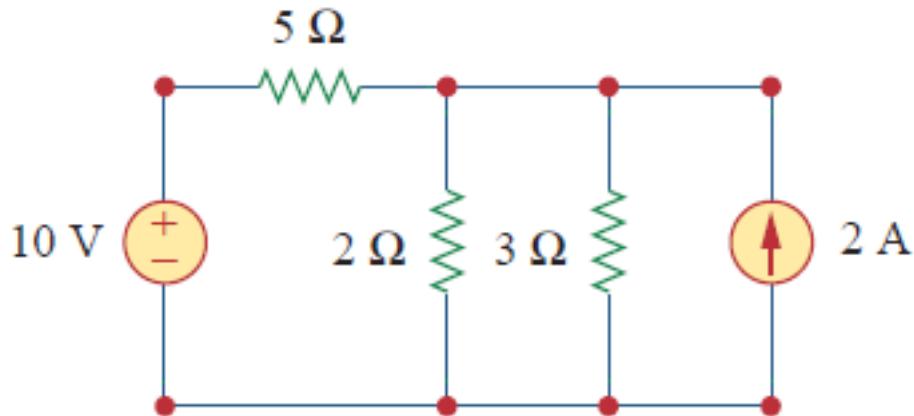
Example

How many nodes and branches are the circuit?



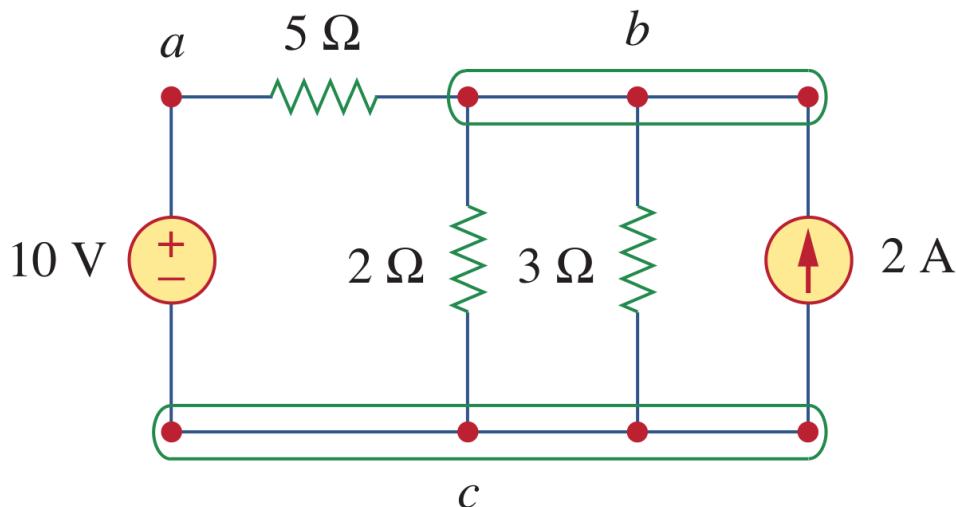
Example

How many nodes and branches are the circuit?



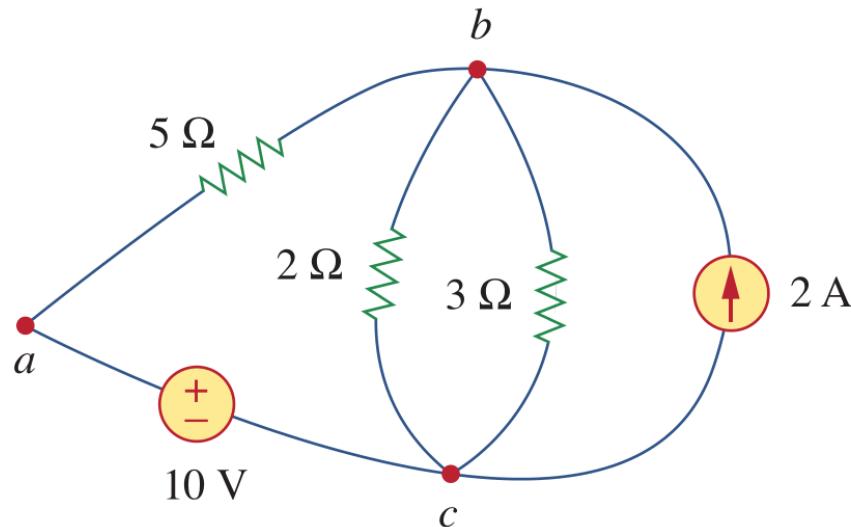Example

How many nodes and branches are the circuit?



Circuit containing 3 nodes and 5 branches


Open and Short Circuits

- An open circuit between A and B means $i = 0$.
- Voltage across an open circuit: any value.
- An open circuit is equivalent to $R = \infty \Omega$.
- A short circuit between A and B means $v = 0$.
- Current through a short circuit: any value.
- A short circuit is equivalent to $R = 0 \Omega$.


Passive Elements (Linear)



$$v = Ri$$

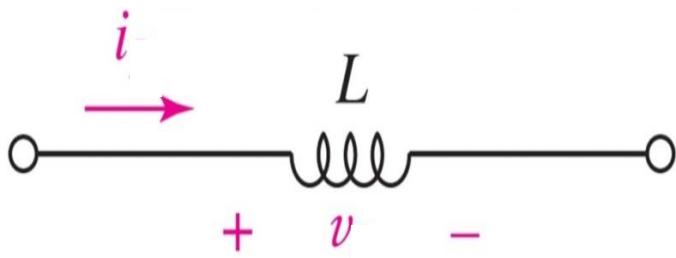


$$v = L \frac{di}{dt}$$

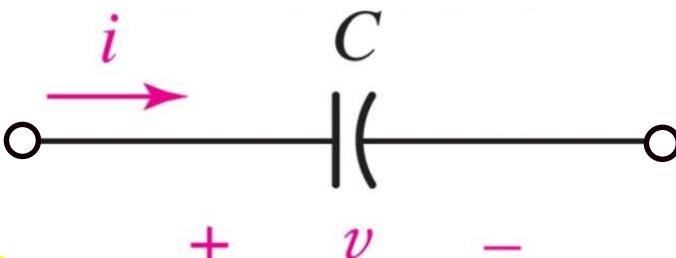

$$i = C \frac{dv}{dt}$$


Kirchhoff's Current Law

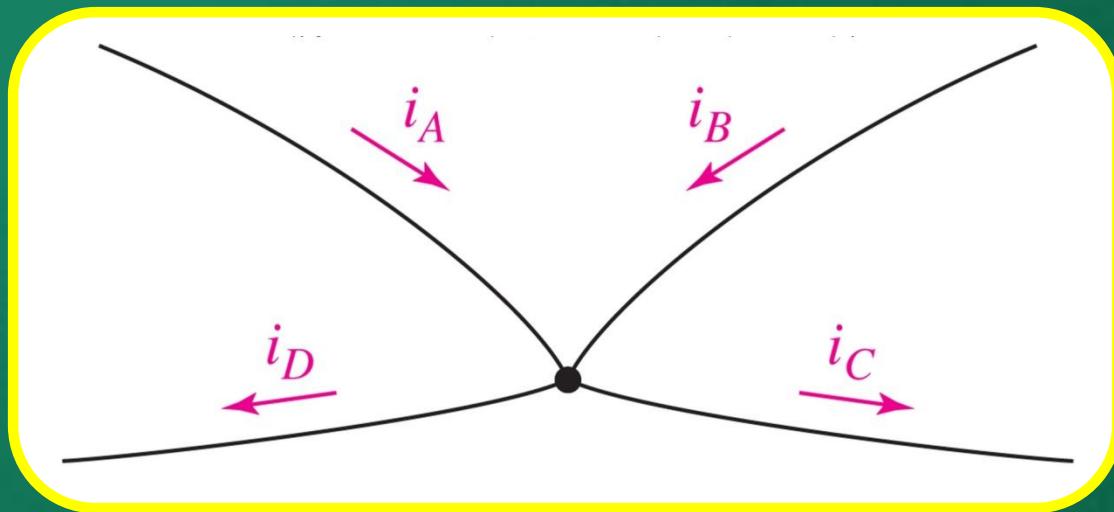KCL - The algebraic sum of the current entering any node is zero.



Kirchhoff's Current Law

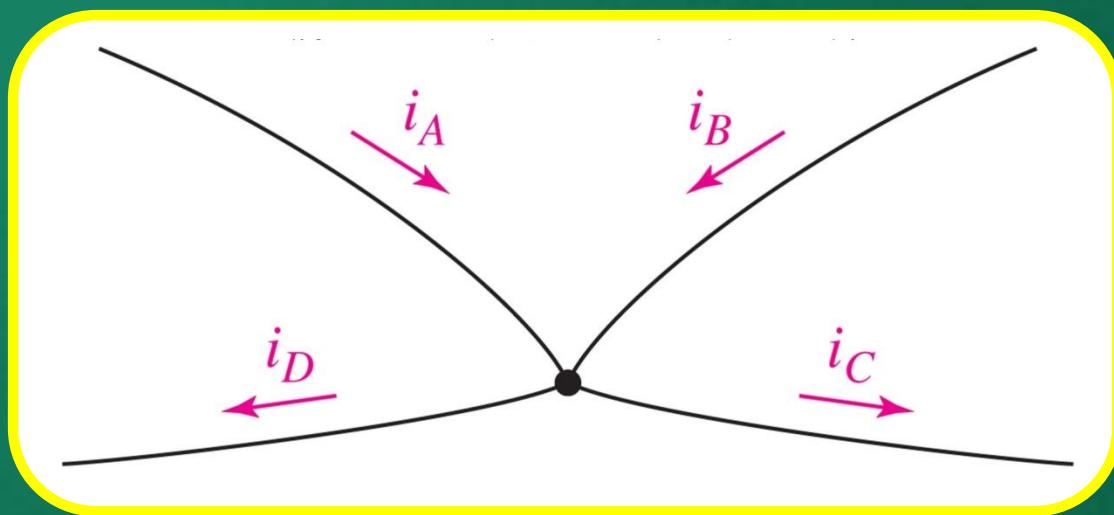KCL - The algebraic sum of the current entering any node is zero.



$$i_A + i_B + (-i_C) + (-i_D) = 0$$

KCL: Alternative Forms

□ Current IN is zero:


$$i_A + i_B + (-i_C) + (-i_D) = 0$$

□ Current OUT is zero:

$$(-i_A) + (-i_B) + i_C + i_D = 0$$


□ Current IN=OUT:

$$i_A + i_B = i_C + i_D$$

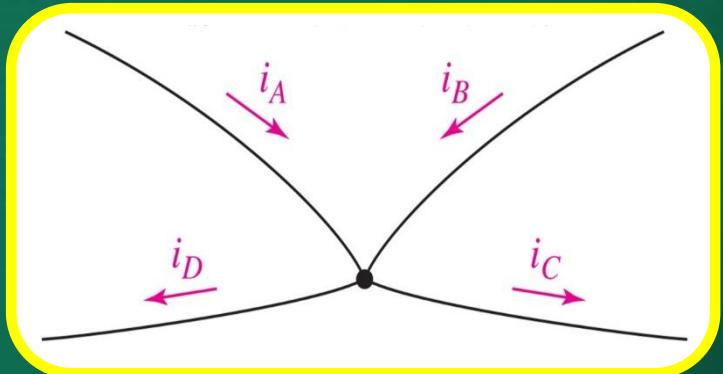

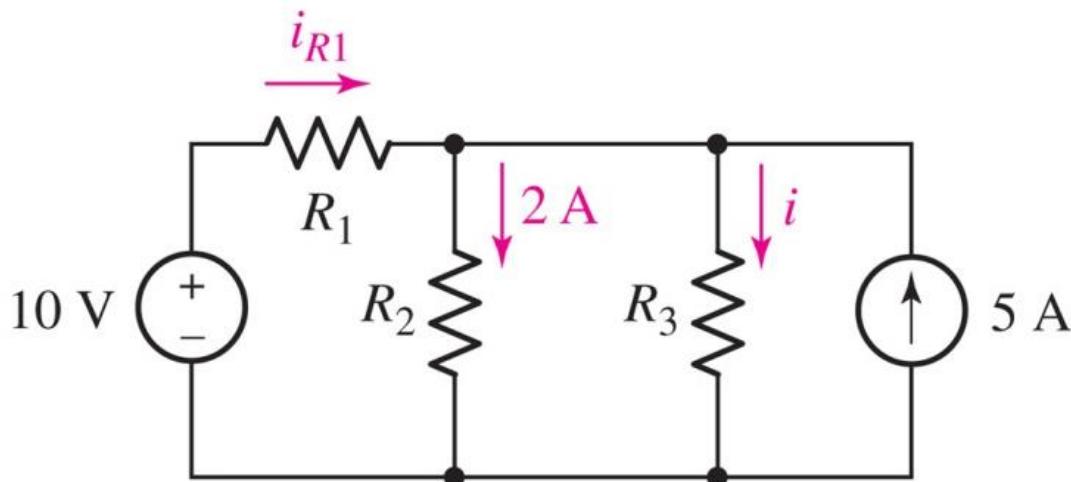
Example: KCL Application

Find the current through resistor R_3 if it is known that the voltage source supplies a current of 3 A.



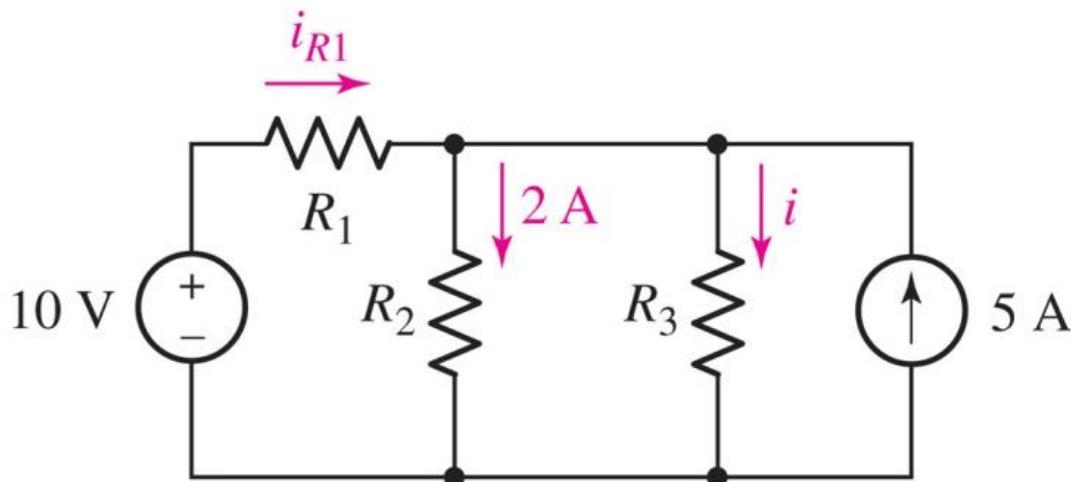Example: KCL Application


Find the current through resistor R_3 if it is known that the voltage source supplies a current of 3 A.



Answer: $i = 6 \text{ A}$

Kirchhoff's Voltage Law

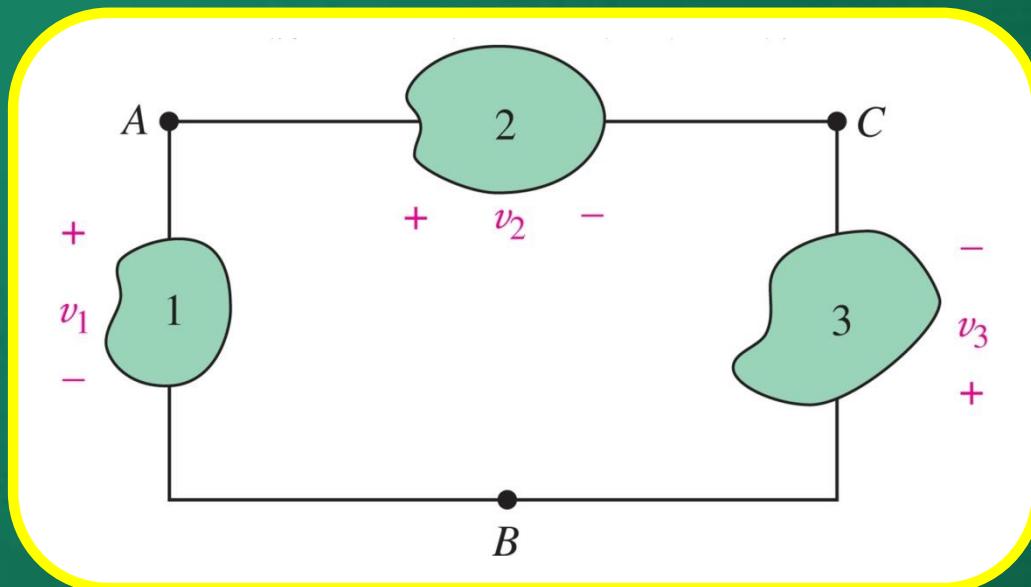KVL - The algebraic sum of the voltages around any closed path is zero.



$$v_1 + (-v_2) + v_3 = 0$$

KVL: Alternative Forms

- Sum of RISES is zero (clockwise from B):


$$v_1 + (-v_2) + v_3 = 0$$

- Sum of DROPS is zero (clockwise from B):

$$(-v_1) + v_2 + (-v_3) = 0$$


- Two paths,
same voltage (A to B)

$$v_1 = v_2 + (-v_3)$$

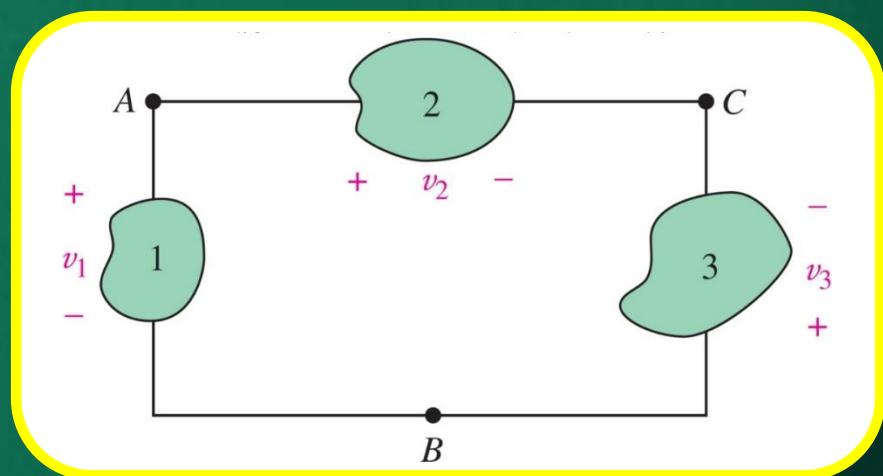

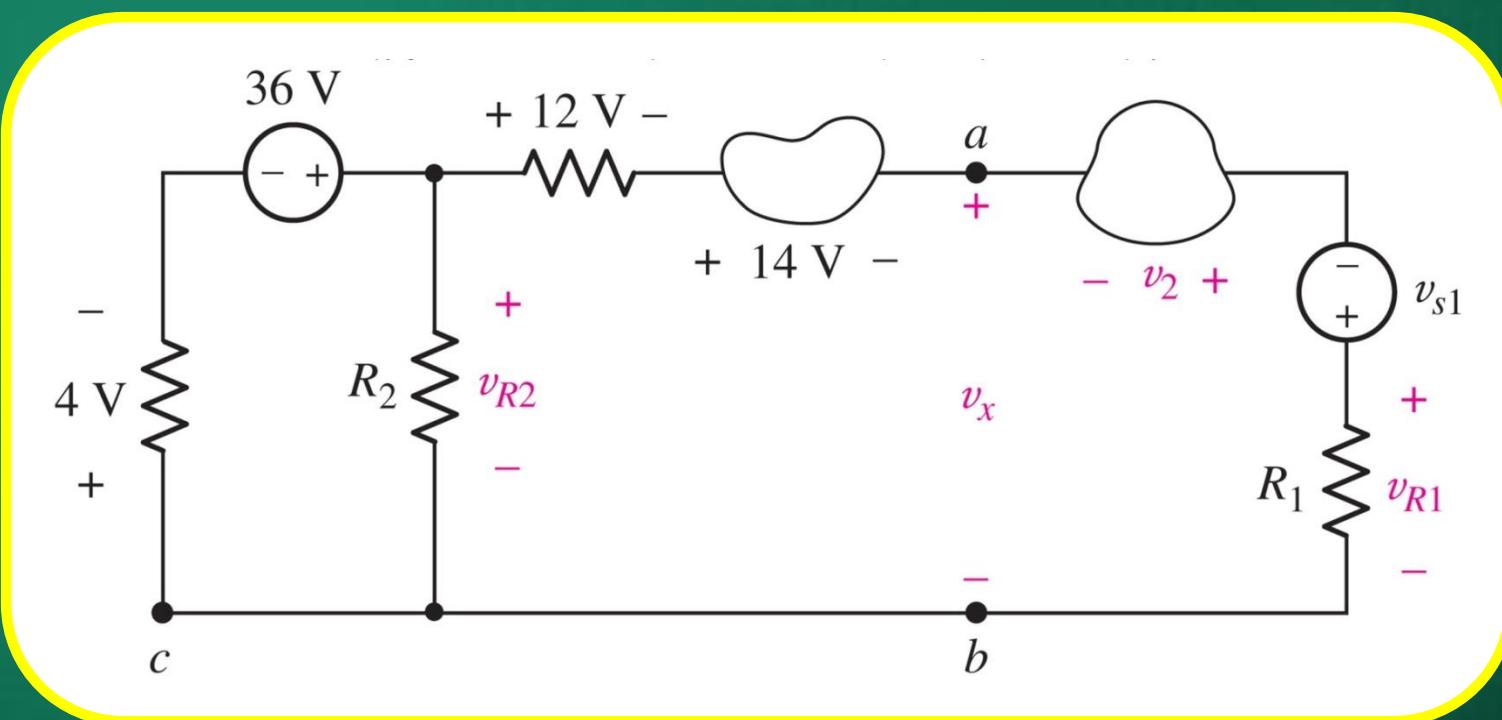
Example: KVL Application

Find v_{R2} (the voltage across R_2) and the voltage v_x .



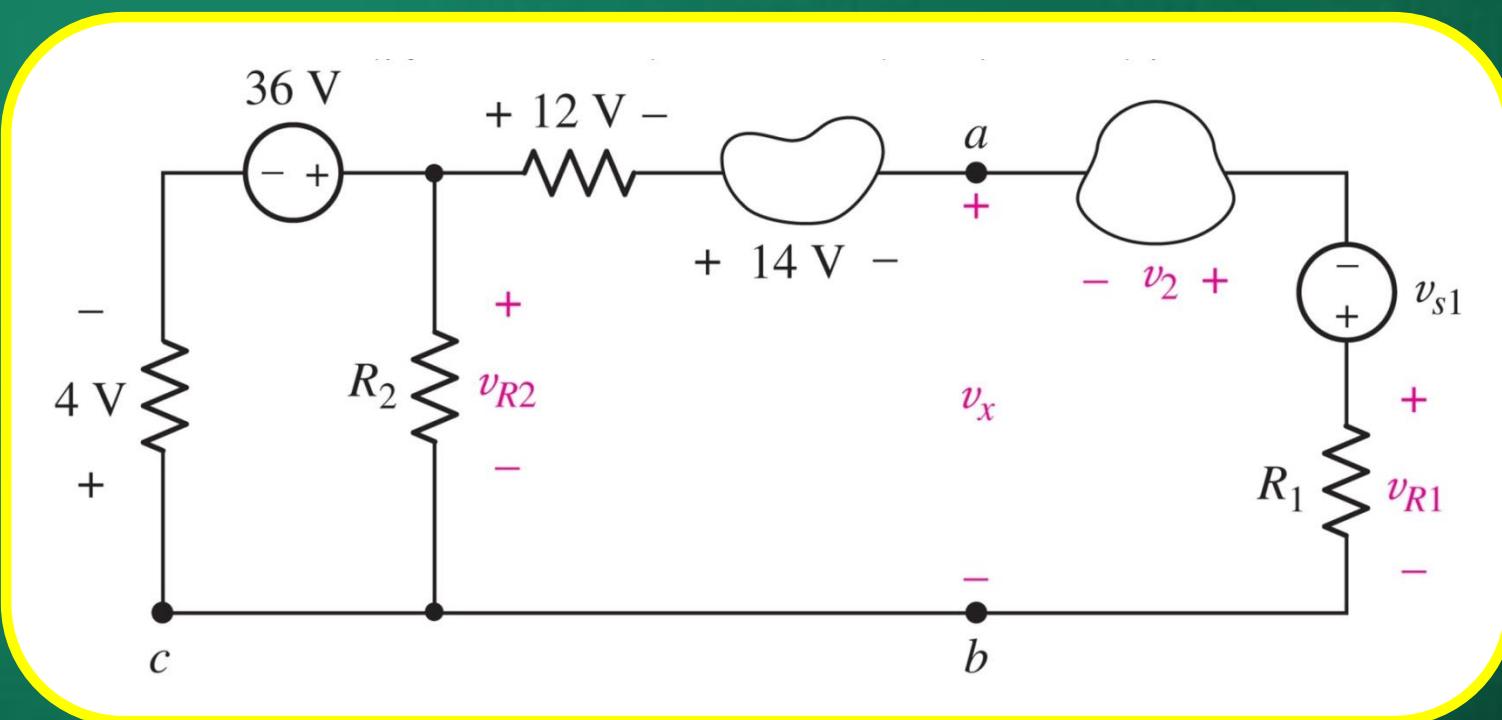Example: KVL Application


Find v_{R2} (the voltage across R_2) and the voltage v_x .



Answer: $v_{R2} = 32 \text{ V}$ and $v_x = 6 \text{ V}$


Applying KVL, KCL, Ohm's Law

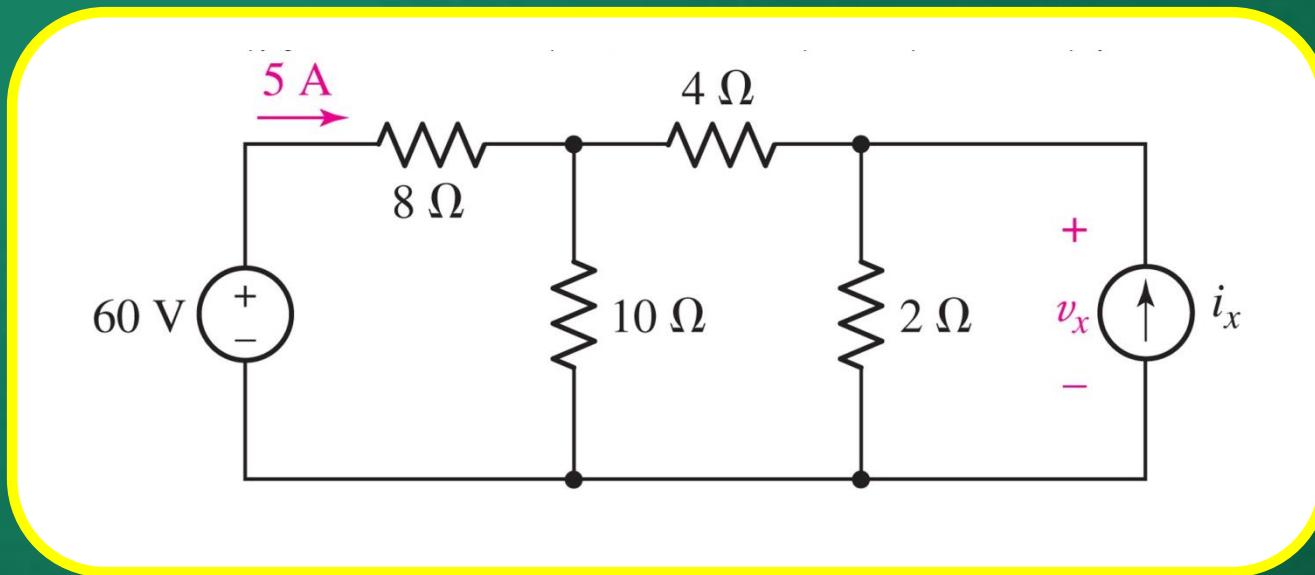Solve for the voltage v_x and the current i_x



Applying KVL, KCL, Ohm's Law

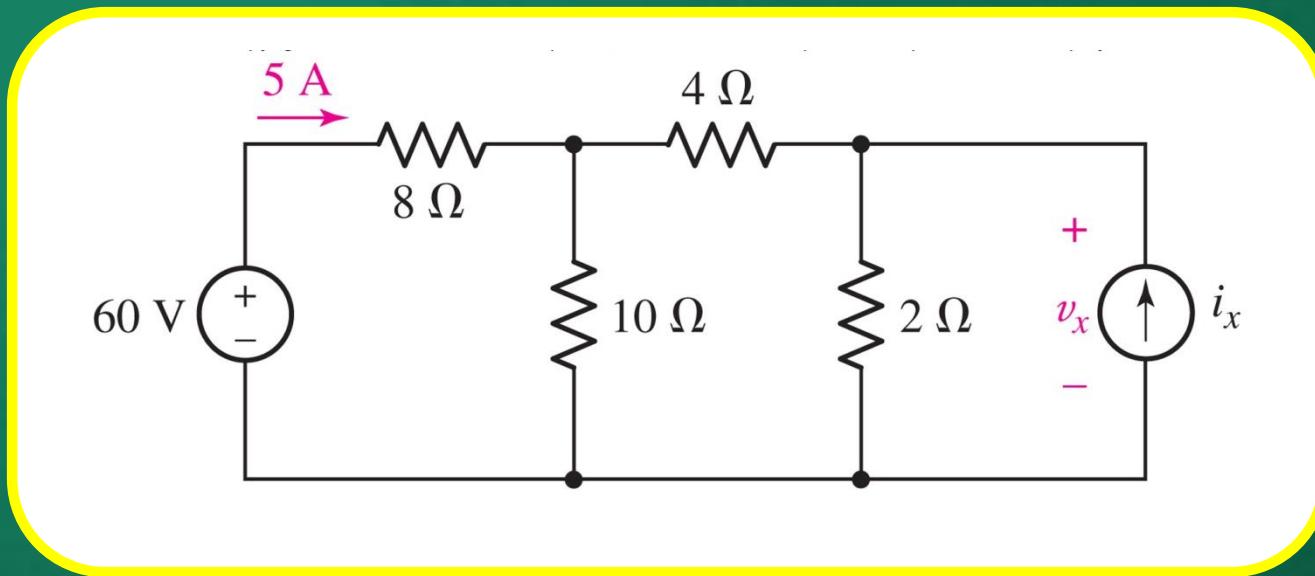
Solve for the voltage v_x and the current i_x



Answer: $v_x = 8 \text{ V}$ and $i_x = 1 \text{ A}$


Series Connections

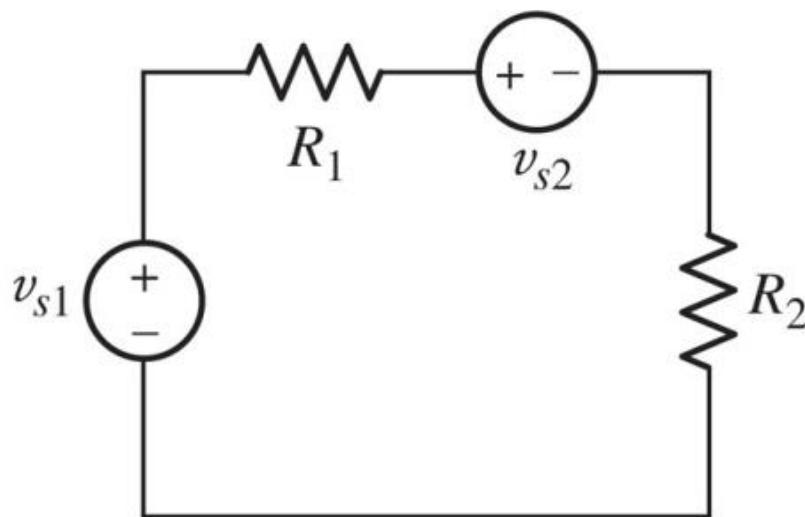Elements in a circuit that carry the same current are said to be connected in series.




Parallel Connections

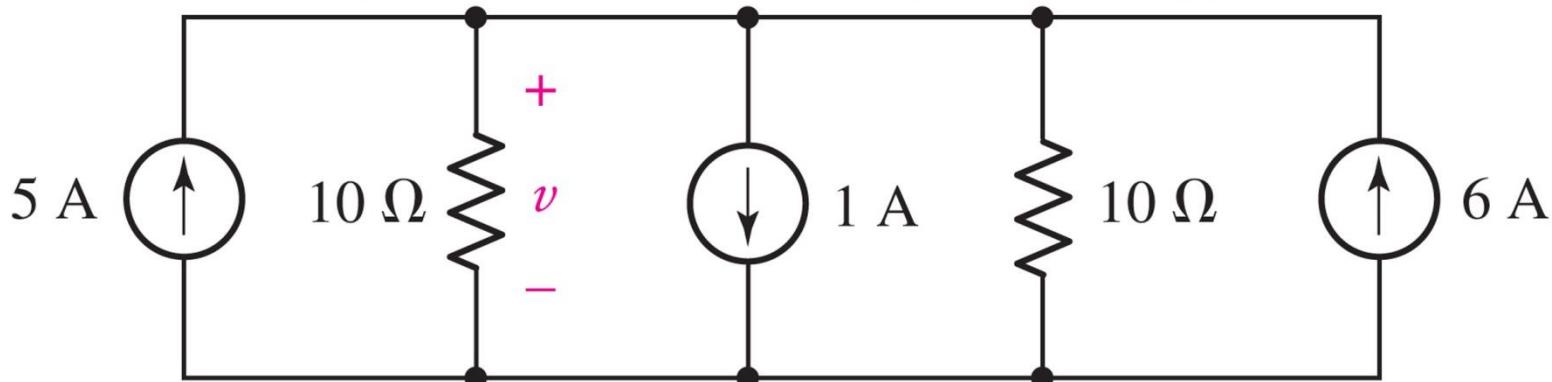Elements in a circuit having a common voltage across them are said to be connected in parallel.



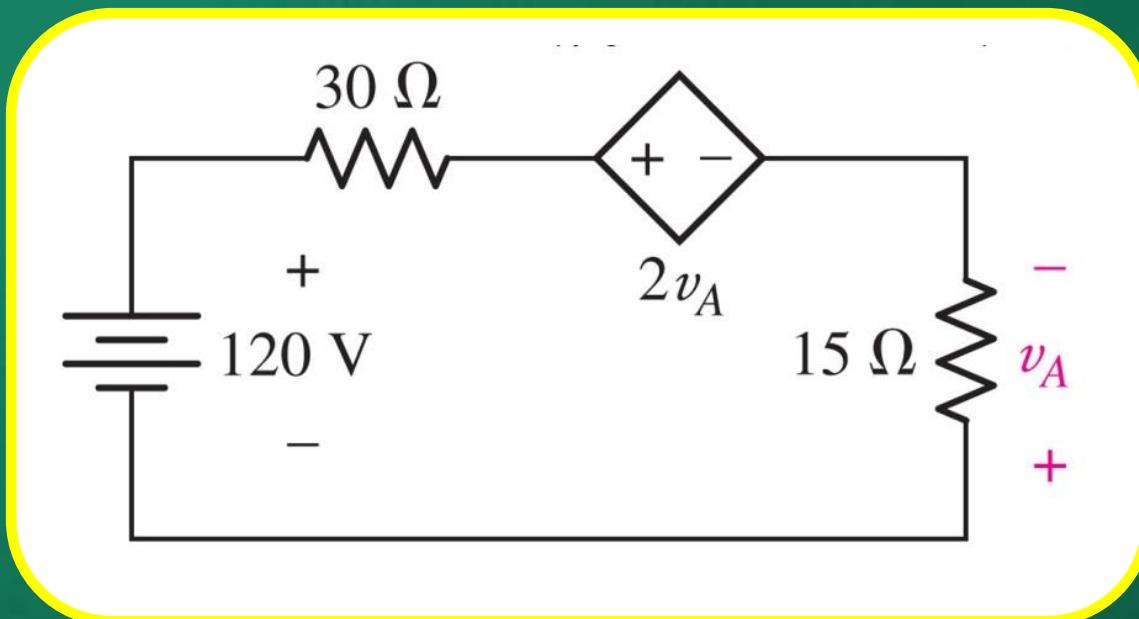
Example: Single Loop Circuit

Calculate the power absorbed by each element.



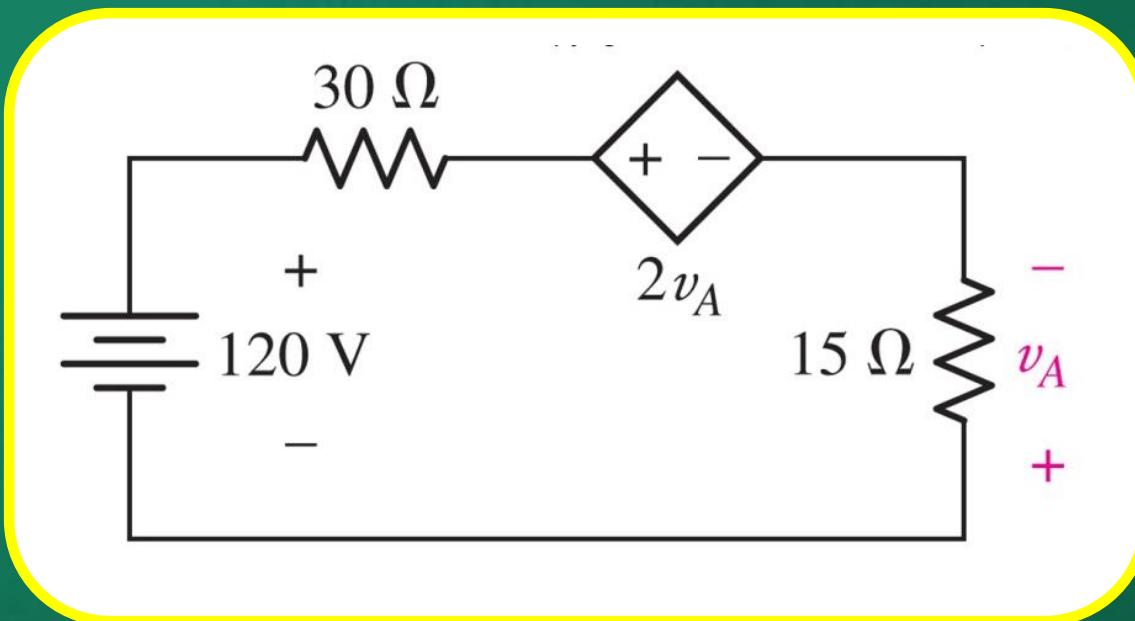Example: Single Loop Circuit


Calculate the power absorbed by each element.



Answer: $P_{120\text{V}} = -960 \text{ W}$, $P_{30} = 1920 \text{ W}$, $P_{\text{dep}} = -1920 \text{ W}$, $P_{15} = 960 \text{ W}$

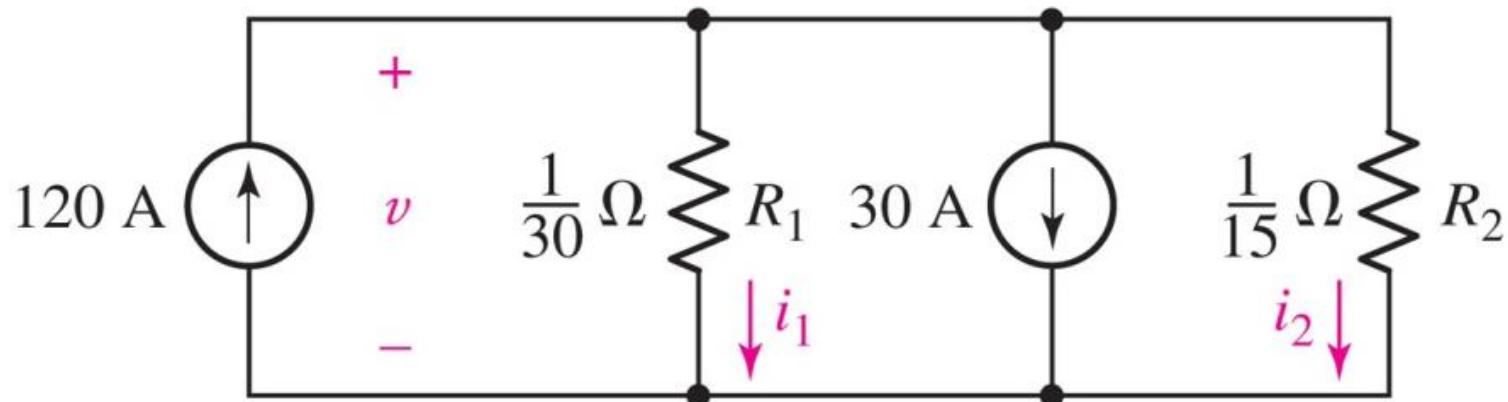
Example: Single Node-Pair Circuit

Find the voltage v and the currents i_1 and i_2 .



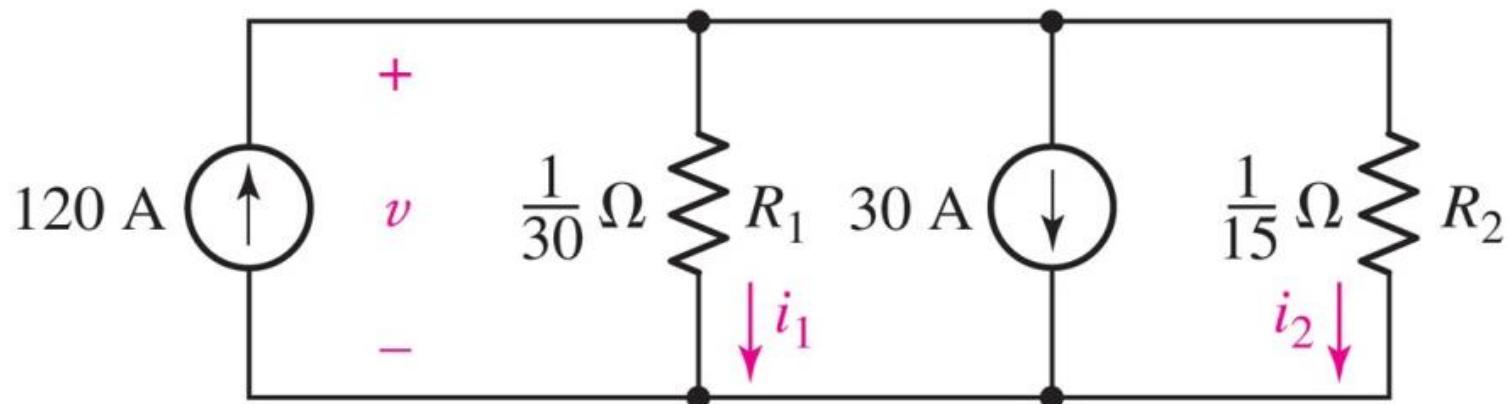Example: Single Node-Pair Circuit


Find the voltage v and the currents i_1 and i_2 .



Answer: $v = 2$ V, $i_1 = 60$ A, and $i_2 = 30$ A


Ex: Single Node-Pair Circuit

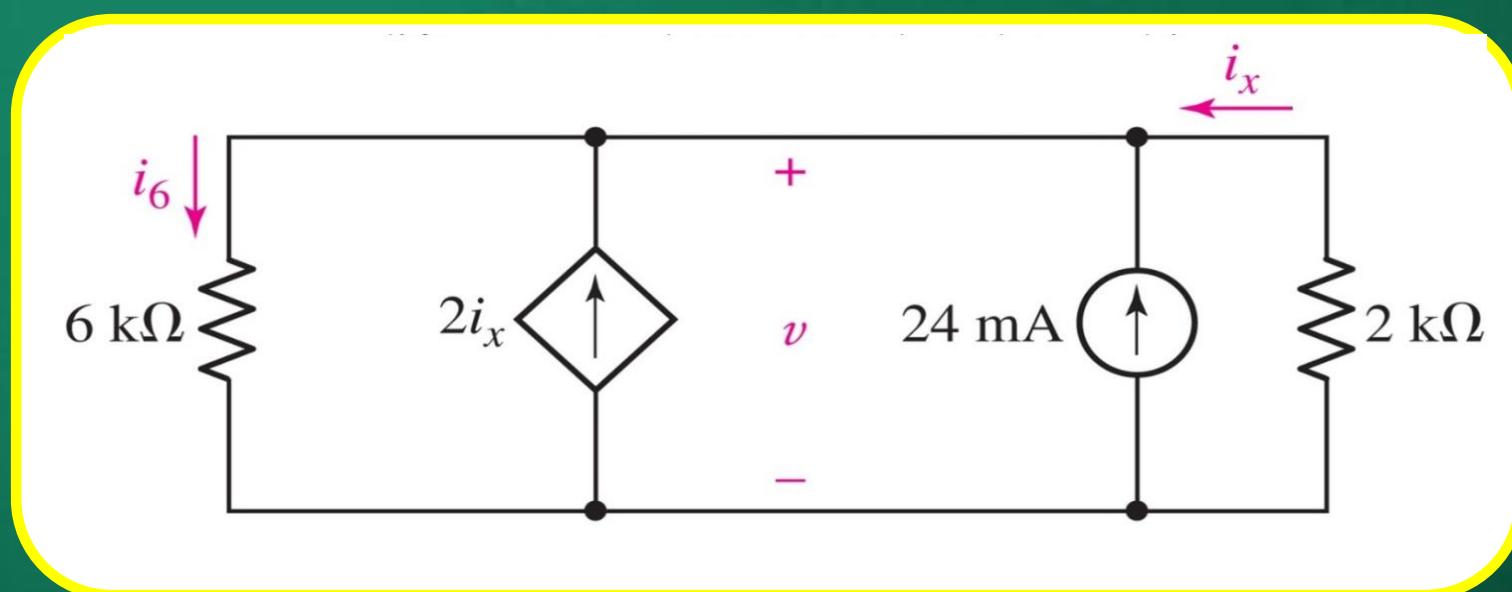Determine the value of v and the power supplied by the independent current source.



Ex: Single Node-Pair Circuit

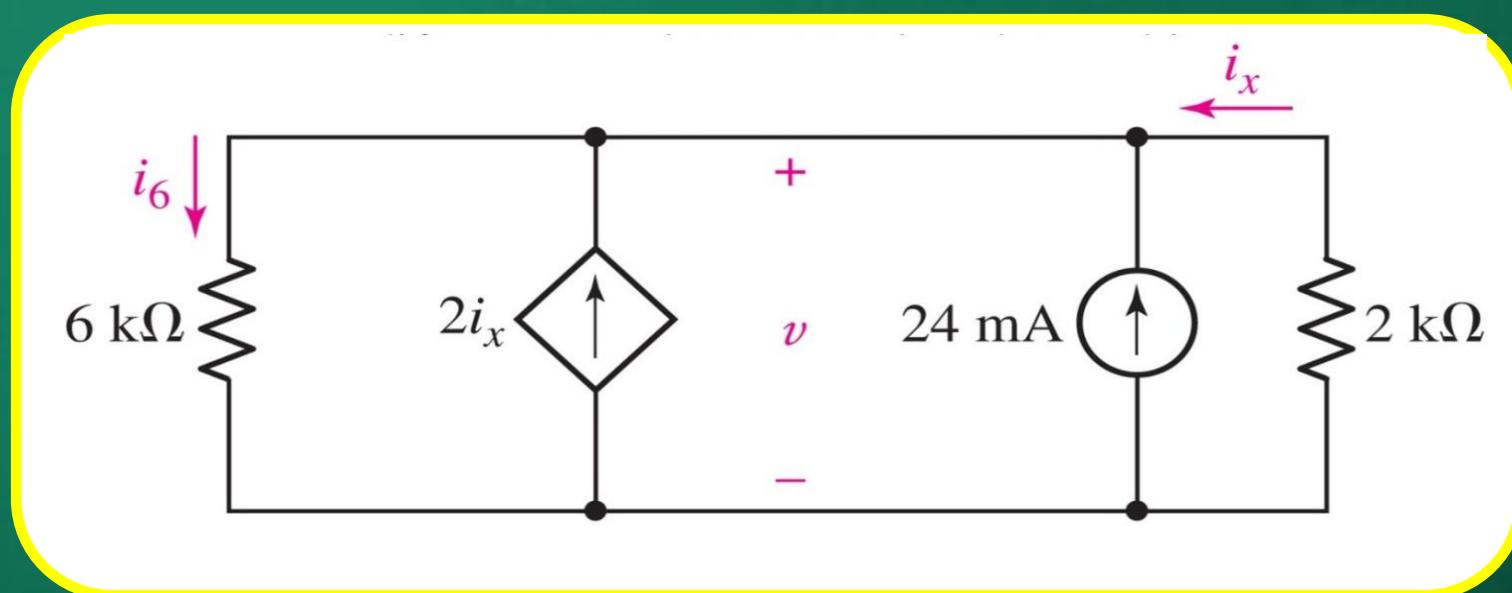
Determine the value of v and the power supplied by the independent current source.



Answer: $v = 14.4 \text{ V}$, $P_{24\text{mA}} = 345.6 \text{ mW}$


Example

Determine the value of v_o and i .

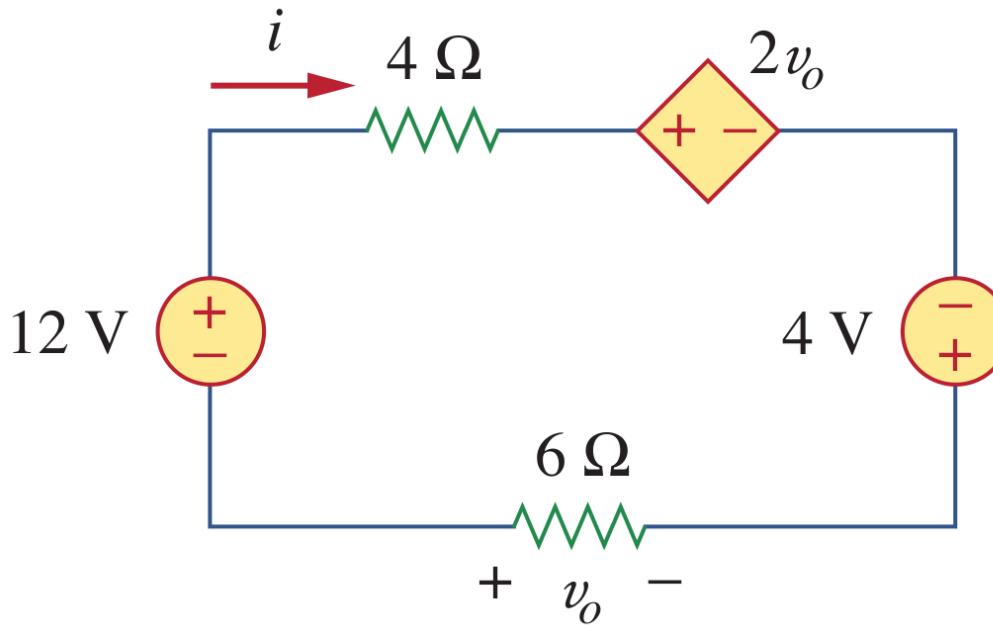

Example


Determine the value of v_o and i .

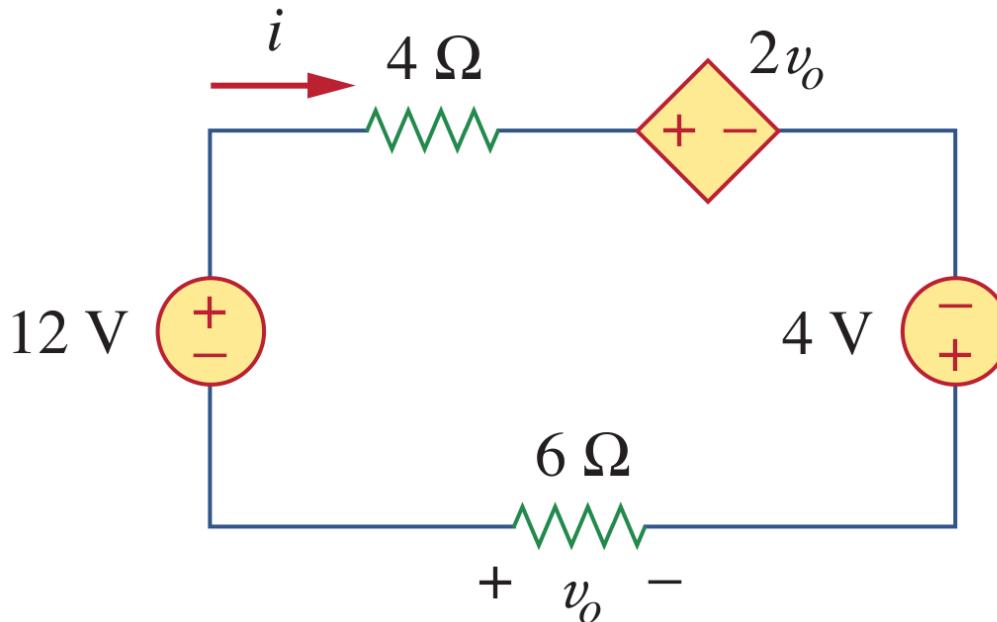


Answer: $v_o = 48 \text{ V}$, $i = -8 \text{ A}$

Impossible Circuits

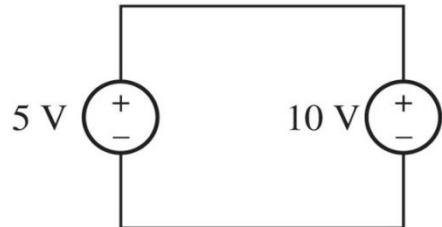
Our circuit models are idealizations that can lead to apparent physical absurdities.



(a)

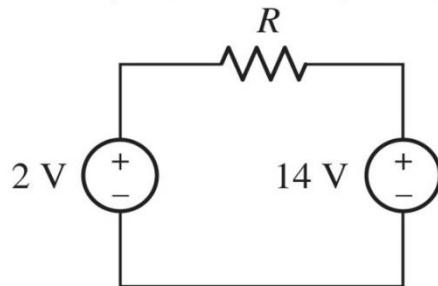


(b)

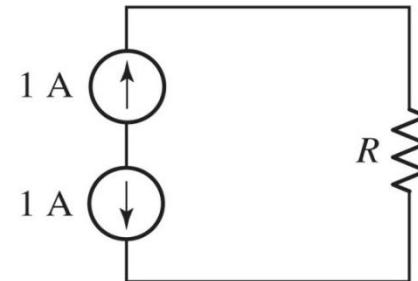


(c)

Impossible Circuits

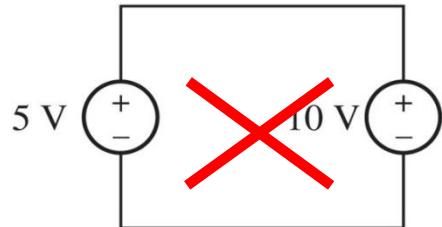
Our circuit models are idealizations that can lead to apparent physical absurdities.



(a)

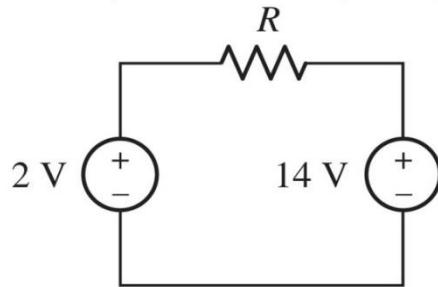


(b)

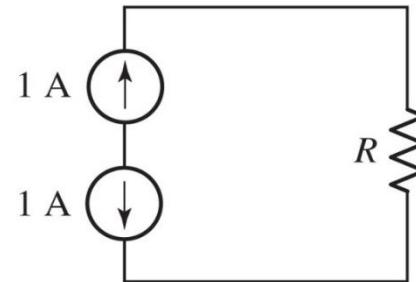


(c)

Impossible Circuits

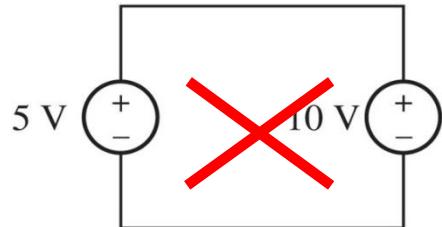
Our circuit models are idealizations that can lead to apparent physical absurdities.



(a)

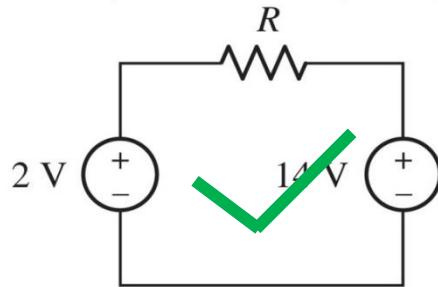


(b)

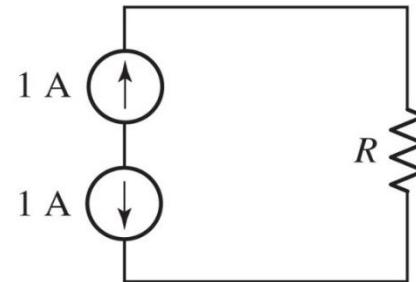


(c)

Impossible Circuits

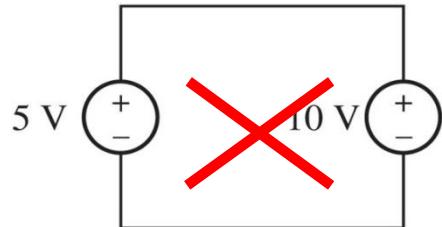
Our circuit models are idealizations that can lead to apparent physical absurdities.



(a)

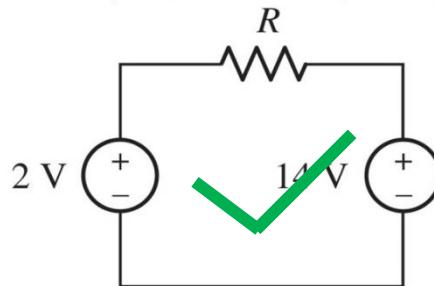


(b)

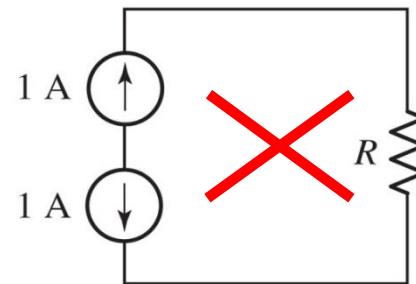

(c)


Series and Parallel Sources

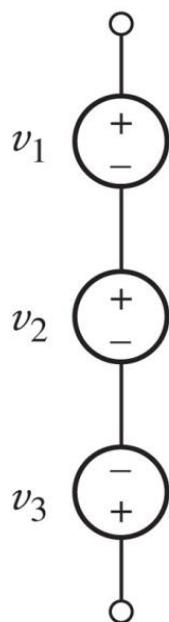Voltage sources connected in series can be combined into an equivalent voltage source.




Series and Parallel Sources

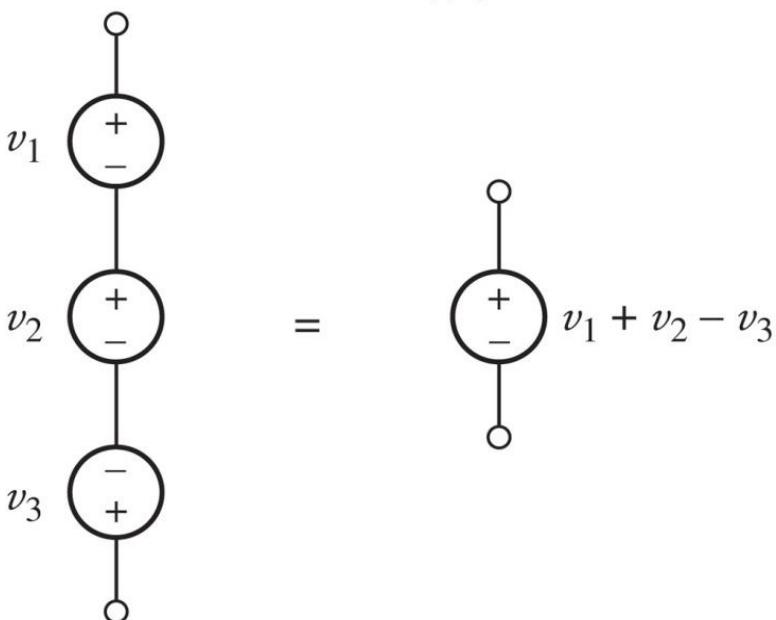Voltage sources connected in series can be combined into an equivalent voltage source.




Series and Parallel Sources

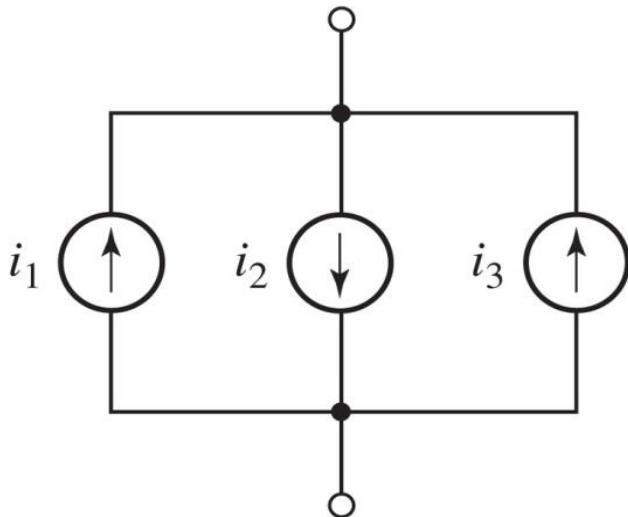Current sources connected in parallel can be combined into an equivalent current source.



Series and Parallel Sources

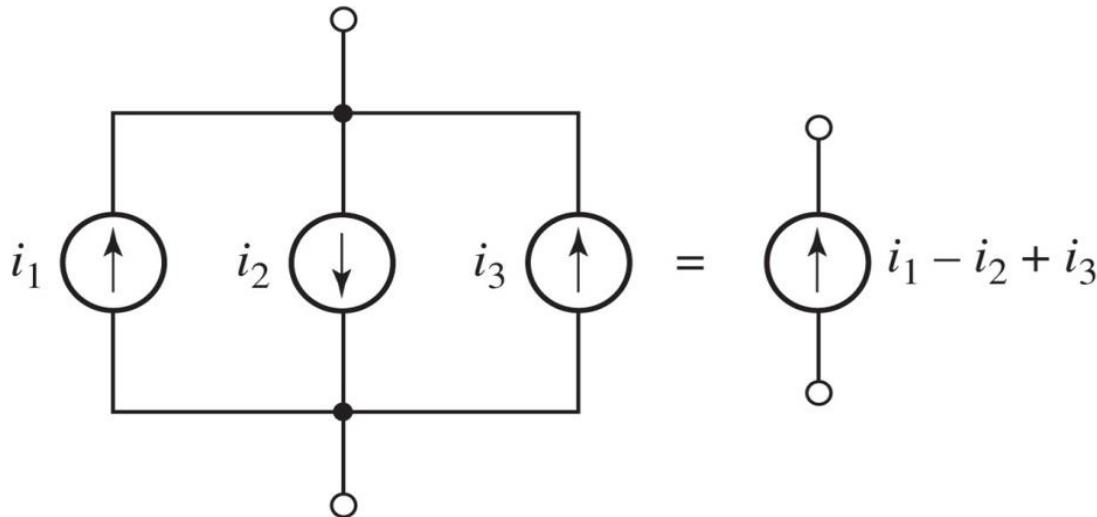Current sources connected in parallel can be combined into an equivalent current source.




Voltage Division

Resistors in series share the voltage applied to them.


Voltage Division

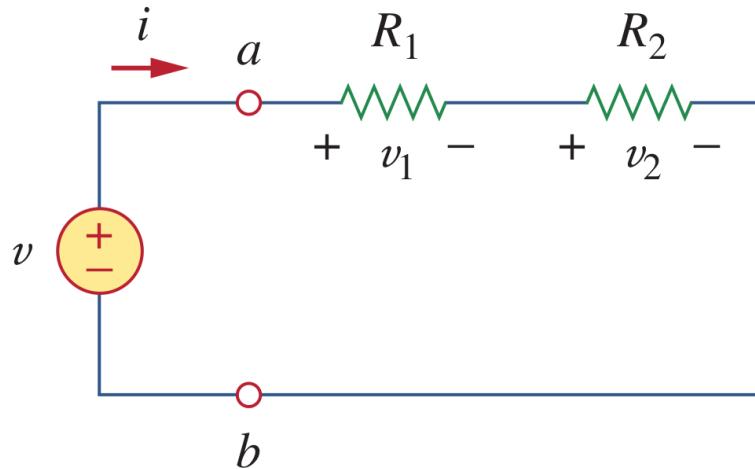Resistors in series share the voltage applied to them.



Voltage Division

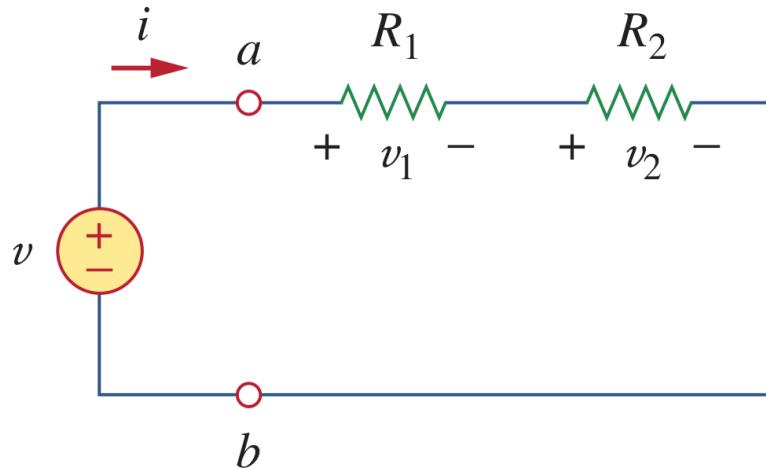
Resistors in series share the voltage applied to them.



$$v_1 = \frac{R_1}{R_1 + R_2} v$$

Voltage Division

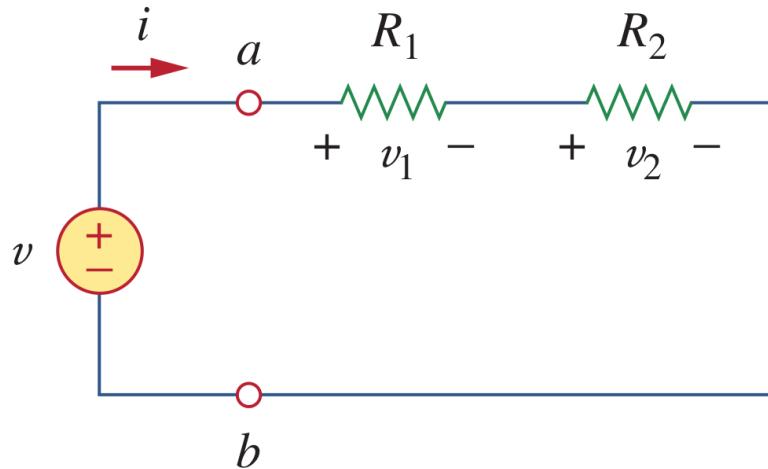Resistors in series share the voltage applied to them.




$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

Voltage Division

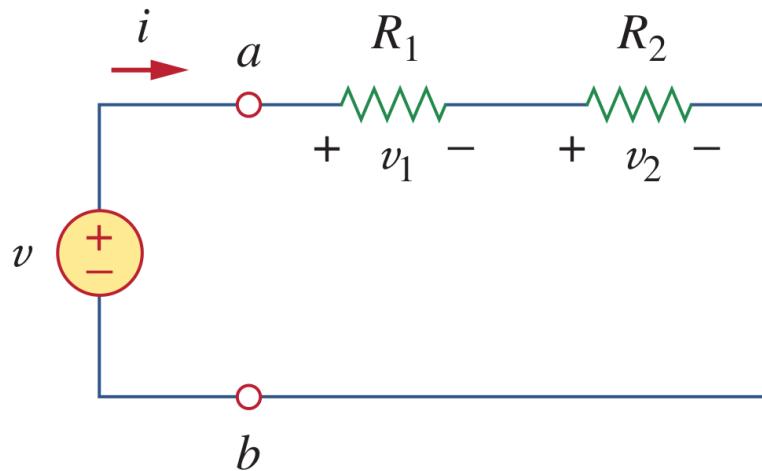Resistors in series share the voltage applied to them.




$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

The voltage across the resistive elements in series will be divided in the ratio of magnitude of the resistances.



Example: Voltage Division

Find v_x

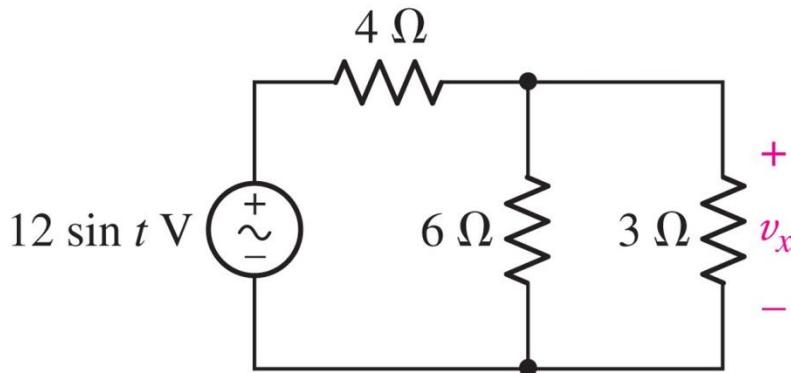



Example: Voltage Division

Find v_x

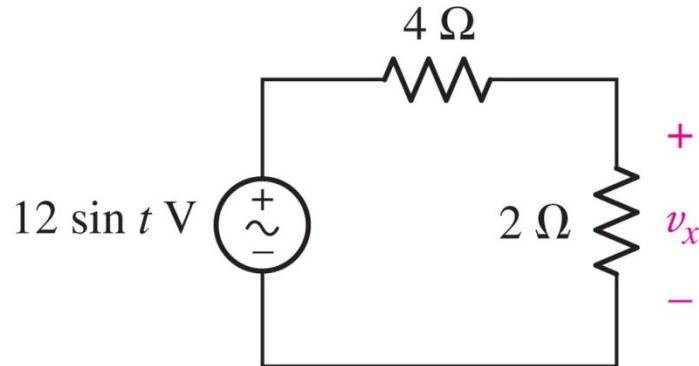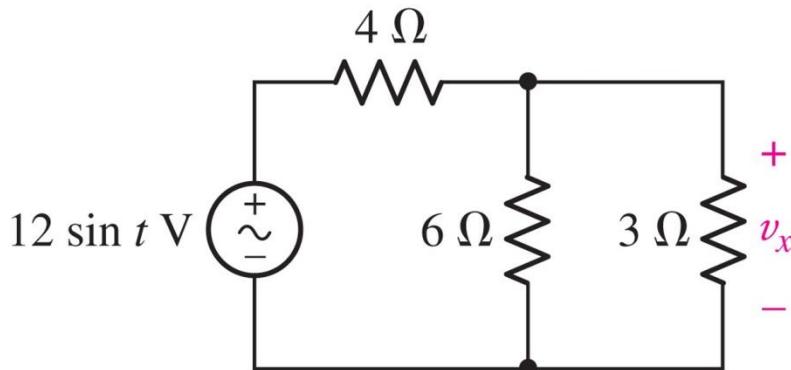

Example: Voltage Division

Find v_x

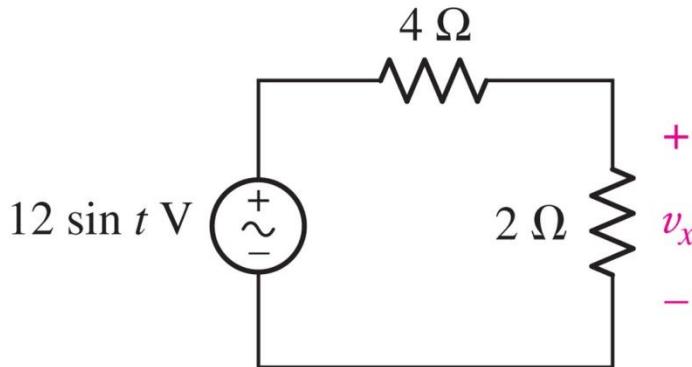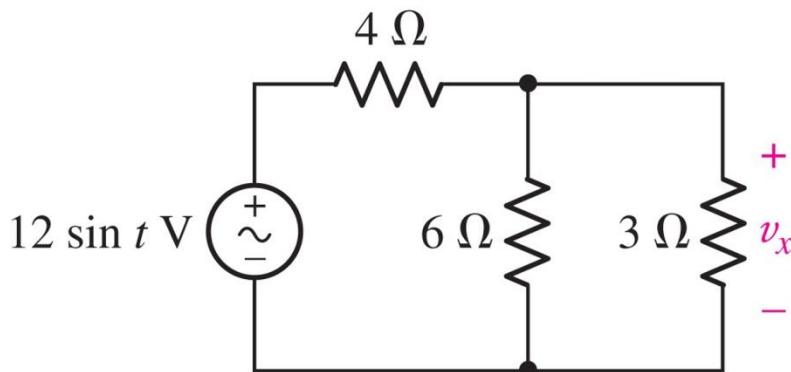


Answer: $v_x(t) = 4 \sin t$ V

Current Division

Resistors in parallel share the current through them.


Current Division

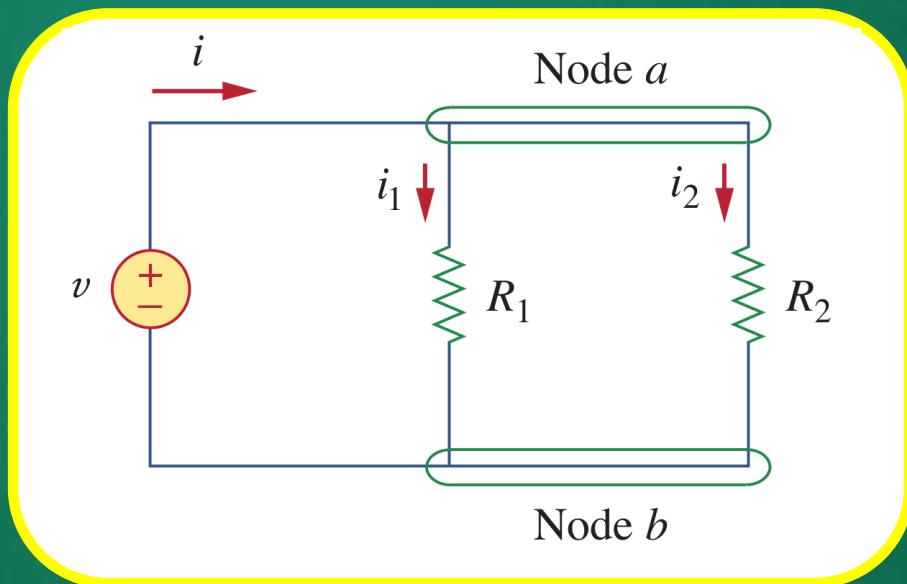Resistors in parallel share the current through them.



Current Division

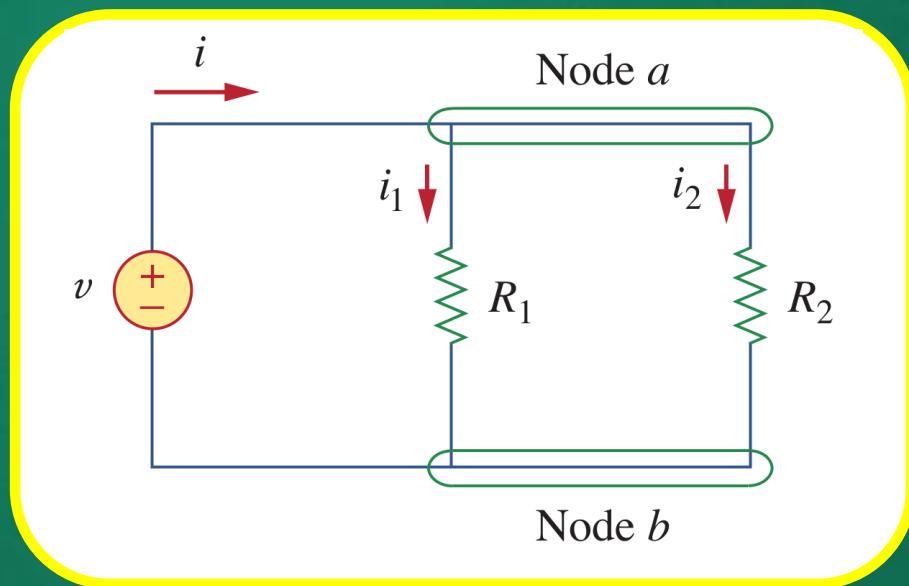
Resistors in parallel share the current through them.



$$i_1 = i \frac{R_2}{R_1 + R_2}$$

Current Division

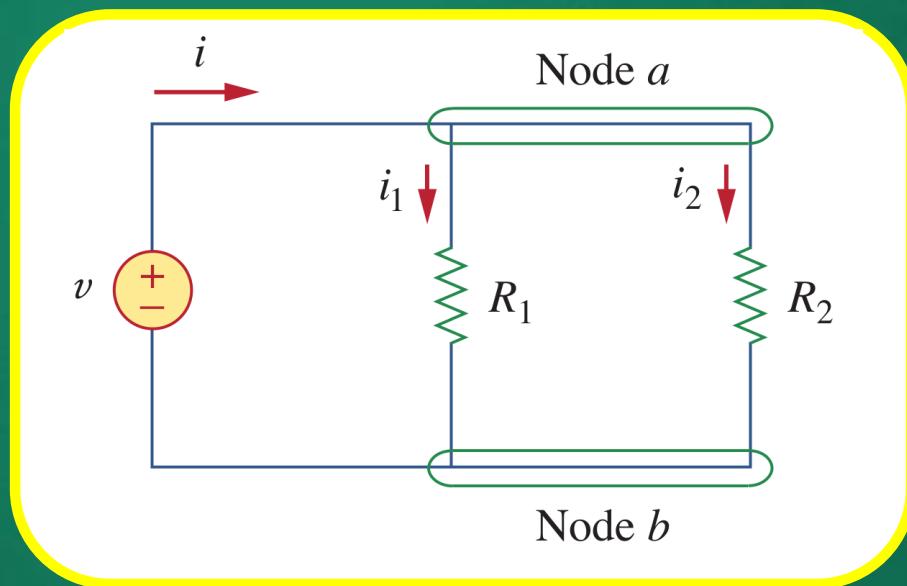Resistors in parallel share the current through them.




$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

Current Division

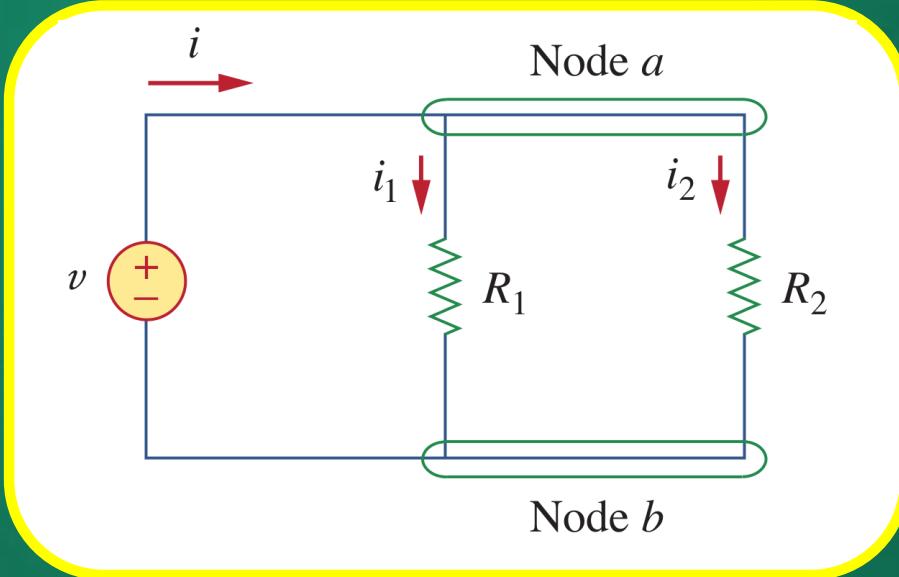Resistors in parallel share the current through them.




$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

The current through resistive elements in parallel will be divided in the ratio of magnitude of the conductances.


Example: Current Division

Find $i_3(t)$

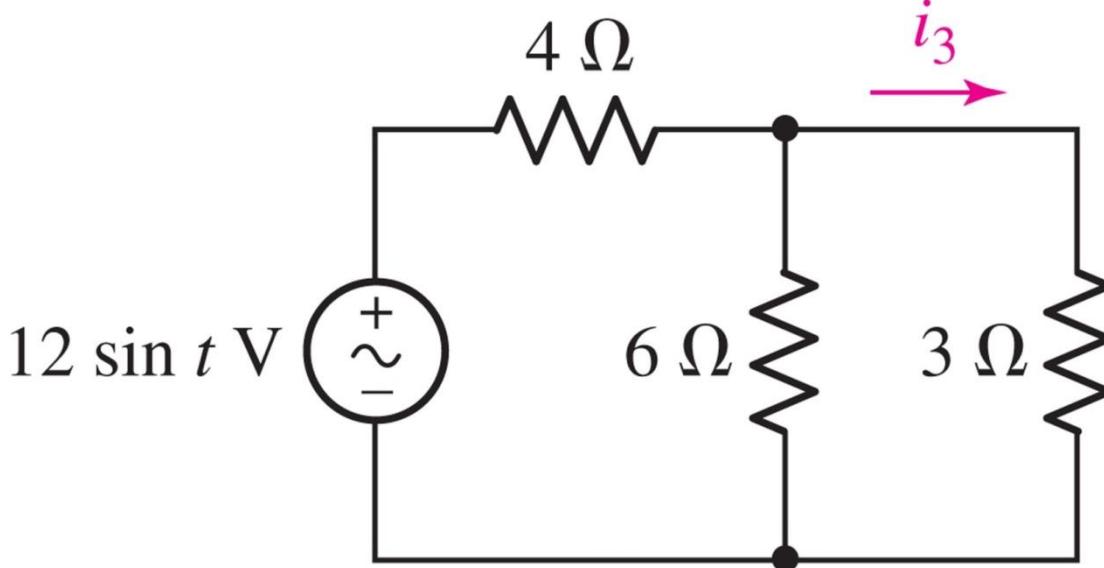


Example: Current Division

Find $i_3(t)$

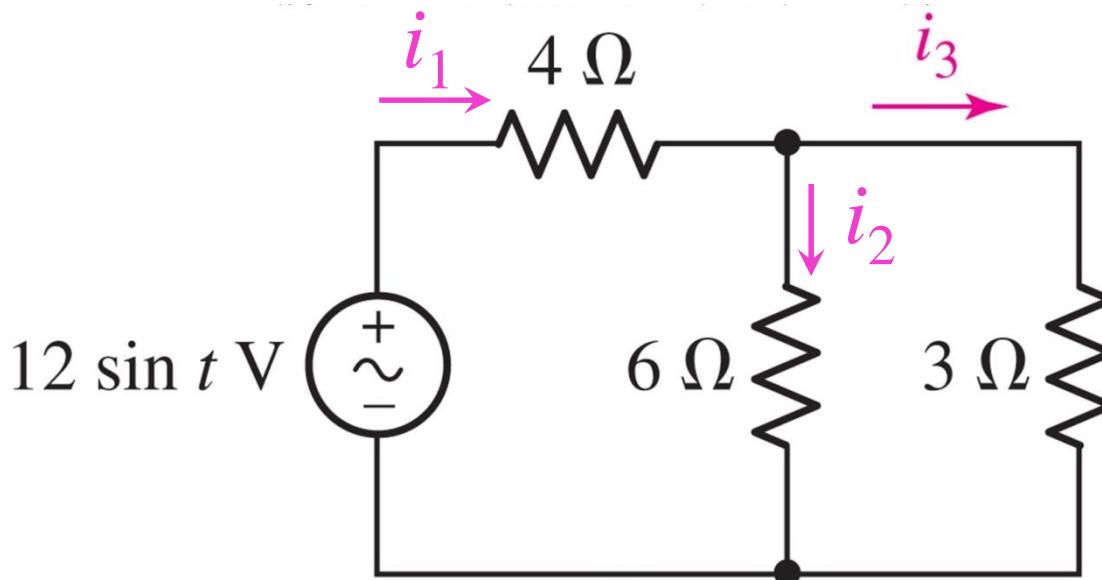

Example: Current Division

Find $i_3(t)$

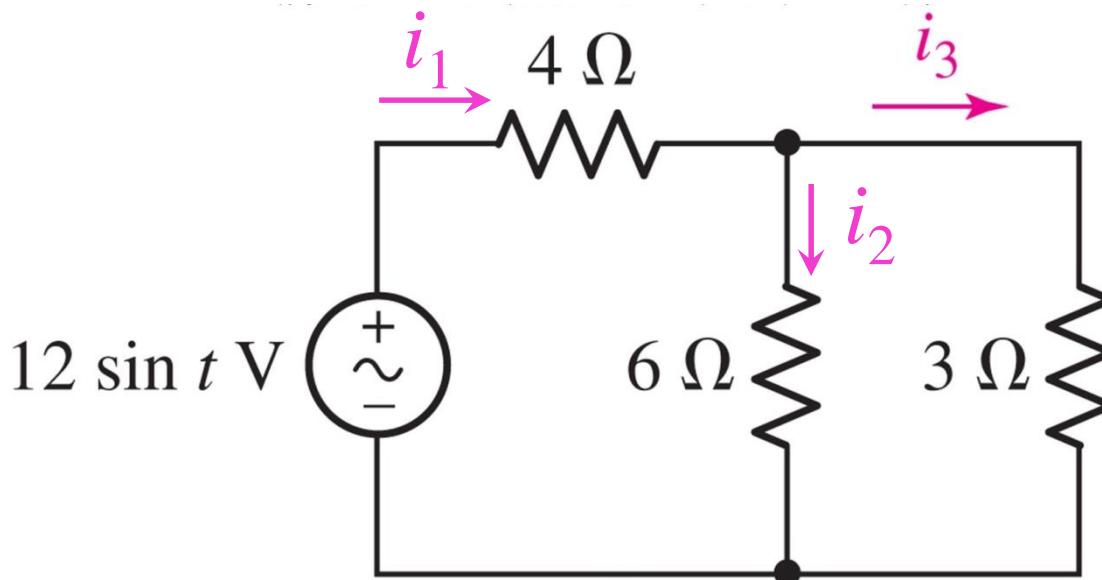

Answer: $i_3(t) = 1.333 \sin t \text{ A}$